

# Basic Principles of HDL Verilog Design

**ECE333 | Digital Systems Laboratory – Professor: Christos Sotiriou**

**Lab Instructor(s): Dimitris Tsalapatas, Nikos Zazatis, Nikos Chatzivangelis,  
Katerina Tsilingiri**

# Outline

---

- Golden Rules
  - Dataflow & FSMs Design
  - Procedural Block Assignments
  - Do **NOT** Infer Latches
  - Reset & Clock Logic
- Hierarchical Module Design & Coding Style


# Golden Rule #1: Dataflow & FSMs Design

---

- Design **Dataflow & FSMs** *prior the implementation process*
- Dataflow:
  - **must be strictly equivalent (1-1)** to the instantiations of top-level module
  - in case of multiple levels in hierarchy,
    - you can provide more detailed info
      - either within the same schematic
      - or with a separate dataflow of the internal hierarchy
- State Machine(s):
  - **Mealy vs Moore** (*upcoming lectures*)
 
# Golden Rule #2: Procedural Block Assignments

- **Sequential vs Combinational** always@block
  - Sequential:
    - *always @(posedge clock or ...)*
      - *posedge clock*, implies the **instantiation of flip-flop(s)**
      - *every other signal in sensitivity list*, implies an **asynchronous control** signal for the flip-flop(s)
      - any signal *not in the sensitivity list* and *used for multiplexing* within the block, implies a
        - **synchronous control** signal for the flip-flop(s)
        - *Rule of thumb: Non-Blocking Assignments (<=)*



# Golden Rule #2: Procedural Block Assignments


- **Sequential vs Combinational** always@block
  - Combinational:
    - *always @(signal\_1 or ... or signal\_x)*
      - sensitivity list must contain **all associated input** signals
        - Rule of thumb: **Blocking Assignments (=)**

**ALWAYS SEPARATE** combinational and sequential logic blocks

Do **NOT MIX** blocking and non-blocking assignments *in the same alwaysblock*


Do **NOT ASSIGN** the same variable *from more than one alwaysblock*

 Do **NOT ASSIGN** as output and **USE** as input a variable *in the same always block*



 
# Golden Rule #2: Blocking VS Non-Blocking


```
always @( posedge clk )
begin
    x = next_x;
end
```



 
```
always @( posedge clk )
begin
    x <= next_x;
end
```


 
```
always @( posedge clk )
begin
    x = next_x;
    y = x;
end
```


 
```
always @( posedge clk )
begin
    x <= next_x;
    y <= x;
end
```



# Golden Rule #3: Do NOT Infer Latches

- **Complete signal state** *for all* cases in Combinational alwaysblock
  - Latches are inferred due to
    - **NOT** assigning Left Hand Side (LHS) for ALL conditions
    - or*
    - **MISSING** signal in the sensitivity list


Every if has a **COMPLEMENTARY** else statement

Every case is **full** and is defined for the **complete state** of the examined input signals

Every if/else/case must **ASSIGN ALL** LHS signals
 
# Golden Rule #4: Reset & Clock Logic

- **NEVER** put logic on the *reset* or *clock*
  - **NEVER MIX** reset types
    - asynchronous vs synchronous reset
  - **NEVER** create clock domain crossings (*upcoming lectures*)
  - Advanced designs have more than one clocks *which they usually run on different frequencies*





# Hierarchical Module Design and Coding Style

- Top-module must contain only module instantiations
  - **NO RTL in top-level**
    - direct wire assignments are allowed
      - e.g.: `assign signalx = signaly;`
- Every module should be in a separate file
  - module header comment segment with a basic functional description
  - I/O ports description
  - utilise parameters or definitions
    - ***localparam*** vs ***parameter*** vs ***`define***
  - for each instantiation/implementation add header comment
    - describe explicit corner cases
- Follow a uniform coding style across all files
  - comments
  - indentations
  - begin-end usage and format *etc.*

# Any Questions?

---

