



# 1<sup>st</sup> Lab Assignment | Overview Report

*ECE333 | Digital Systems Laboratory – Professor: Christos Sotiriou – Dimitris Garyfallou*

*Lab Instructor(s): Nikos Chatzivangelis, Dimitris Tsalapatas, Katerina Tsilingiri, Nikolaos Zazatis, Anastasis Vagenas*

# Overview

---

- ▶ Fundamental Acquired Skills after Completing Lab Assignment 1
  - ▶ Dataflow & Top-level Module (*Golden Rule #1*)
  - ▶ Combinational vs Sequential always blocks (*Golden Rule #2*)
    - ▶ Minimal Implementation with Sequential Elements
  - ▶ Reset & Clock Logic (*Golden Rule #4*)
- ▶ Review Implementation Faults
  - ▶ Hierarchical Design, Coding Style & Comments
  - ▶ Combinational Logic Reset
  - ▶ Anode Driver Refresh Period
  - ▶ Debouncer
  - ▶ MMCM Reset
  - ▶ MMCM Feedback
  - ▶ MMCM VCO Minimum Frequency
  - ▶ Registers' Memory vs FPGA ROM
  - ▶ XDC Constraints Usage & Justification
- ▶ Fundamental Acquired Skills after Completing Lab Assignment 2
  - ▶ FSMs
  - ▶ Testbench
  - ▶ Satisfy Timing Requirements

# Overview

---

## ▶ Fundamental Acquired Skills after Completing Lab Assignment 1

- ▶ Dataflow & Top-level Module (*Golden Rule #1*)
- ▶ Combinational vs Sequential always blocks (*Golden Rule #2*)
  - ▶ Minimal Implementation with Sequential Elements
- ▶ Reset & Clock Logic (*Golden Rule #4*)

## ▶ Review Implementation Faults

- ▶ Hierarchical Design, Coding Style & Comments
- ▶ Combinational Logic Reset
- ▶ Anode Driver Refresh Period
- ▶ Debouncer
- ▶ MMCM Reset
- ▶ MMCM Feedback
- ▶ MMCM VCO Minimum Frequency
- ▶ Registers' Memory vs FPGA ROM
- ▶ XDC Constraints Usage & Justification

## ▶ Fundamental Acquired Skills after Completing Lab Assignment 2

- ▶ FSMs
- ▶ Testbench
- ▶ Satisfy Timing Requirements

# Golden Rule #1: Dataflow Design

---

- ▶ Design **Dataflow** *prior the implementation process*

- ▶ **Dataflow:**

- ▶ **must be strictly equivalent (1-1)** to the instantiations of top-level module
- ▶ in case of multiple levels in hierarchy,
  - you can provide more detailed info
    - either within the same schematic
    - or with a separate dataflow of the internal hierarchy

**! Do not** implement dataflow on hand, use a drawing tool like [drawio](#)

# Golden Rule #2: Procedural Block Assignments

## ► Sequential vs Combinational `always@` block

### ► Sequential:

#### ► `always @(posedge clock or ...)`

- `posedge clock`, implies the **instantiation of flip-flop(s)**
- *every other signal in sensitivity list*, implies an **asynchronous control** signal for the flip-flop(s)
- *any signal not in the sensitivity list and used for multiplexing within the block*, implies a **synchronous control** signal for the flip-flop(s)
  - Rule of thumb: **Non-Blocking Assignments** (`<=`)

### ► Combinational:

#### ► `always @(signal_1 or ... or signal_x)`

- sensitivity list must contain **all associated input** signals
  - Rule of thumb: **Blocking Assignments** (`=`)

**Minimal Implementation with Sequential Elements**

- always reconsider whether you can eliminate some of the instantiated sequential logic

❖ **ALWAYS SEPARATE** combinational and sequential logic blocks

- ❖ Do **NOT MIX** blocking and non-blocking assignments *in the same `always` block*
- ❖ Do **NOT ASSIGN** the same variable *from more than one `always` block*
- ❖ Do **NOT ASSIGN** as output and **USE** as input a variable *in the same `always` block*

# Which one is better?



```
1
2 module anodes_mux();
3
4     // multiplexer for anodes
5     always @(posedge clk or posedge reset)
6     begin
7         case (counter_digit)
8             4'b0010: begin // digit 0
9                 an = 4'b1110;
10            end
11            4'b0110: begin // digit 1
12                an = 4'b1101;
13            end
14            4'b1010: begin // digit 2
15                an = 4'b1011;
16            end
17            4'b1110: begin // digit 3
18                an = 4'b0111;
19            end
20            default: begin // default all digits are off
21                an = 4'b1111;
22            end
23        endcase
24    end
25
26 endmodule
```



```
1 module anodes_mux();
2
3     // multiplexer for anodes
4     always @(counter_digit)
5     begin
6         case (counter_digit)
7             4'b0010: begin // digit 0
8                 an = 4'b1110;
9             end
10            4'b0110: begin // digit 1
11                an = 4'b1101;
12            end
13            4'b1010: begin // digit 2
14                an = 4'b1011;
15            end
16            4'b1110: begin // digit 3
17                an = 4'b0111;
18            end
19            default: begin // default all digits are off
20                an = 4'b1111;
21            end
22        endcase
23    end
24
25 endmodule
```

# Which one is better?



```
1
2 module anodes_mux();
3
4 // multiplexer for anodes
5 always @(posedge clk or posedge reset)
6 begin
7     case (counter_digit)
8         4'b0010: begin // digit 0
9             an = 4'b1110;
10        end
11        4'b0110: begin // digit 1
12            an = 4'b1101;
13        end
14        4'b1010: begin // digit 2
15            an = 4'b1011;
16        end
17        4'b1110: begin // digit 3
18            an = 4'b0111;
19        end
20        default: begin // default all digits are off
21            an = 4'b1111;
22        end
23    endcase
24 end
25
26 endmodule
```



```
1 module anodes_mux();
2
3 // multiplexer for anodes
4 always @(counter_digit)
5 begin
6     case (counter_digit)
7         4'b0010: begin // digit 0
8             an = 4'b1110;
9         end
10        4'b0110: begin // digit 1
11            an = 4'b1101;
12        end
13        4'b1010: begin // digit 2
14            an = 4'b1011;
15        end
16        4'b1110: begin // digit 3
17            an = 4'b0111;
18        end
19        default: begin // default all digits are off
20            an = 4'b1111;
21        end
22    endcase
23 end
24
25 endmodule
```

# Golden Rule #4: Reset & Clock Logic

---

- ▶ **NEVER** put logic on the *reset* or *clock*
  - ▶ **NEVER MIX** reset types
    - ▶ asynchronous vs synchronous reset
  - ▶ **NEVER** create clock from custom combinational logic
    - ▶ In case you think you should a custom combinational signal
      - *probably that signal should be a clock enable*
  - ▶ **NEVER** create clock domain crossings (*studied in more advanced courses*)
    - ▶ Advanced designs have more than one clock
      - *which they usually run on different frequencies*



# Overview

---

- ▶ Fundamental Acquired Skills after Completing Lab Assignment 1
  - ▶ Dataflow & Top-level Module (*Golden Rule #1*)
  - ▶ Combinational vs Sequential always blocks (*Golden Rule #2*)
    - ▶ Minimal Implementation with Sequential Elements
  - ▶ Reset & Clock Logic (*Golden Rule #4*)
- ▶ Review Implementation Faults
  - ▶ Hierarchical Design, Coding Style & Comments
  - ▶ Combinational Logic Reset
  - ▶ Anode Driver Refresh Period
  - ▶ Debouncer
  - ▶ MMCM Reset
  - ▶ MMCM Feedback
  - ▶ MMCM VCO Minimum Frequency
  - ▶ Registers' Memory vs FPGA ROM
  - ▶ XDC Constraints Usage & Justification
- ▶ Fundamental Acquired Skills after Completing Lab Assignment 2
  - ▶ FSMs
  - ▶ Testbench
  - ▶ Satisfy Timing Requirements

# Hierarchical Design, Coding Style & Comments

- ▶ Top-module must contain only module instantiations
  - ▶ **NO RTL in top-level**
    - ▶ direct wire assignments are allowed
      - e.g.: `assign signalx = signaly;`
- ▶ Every module should be in a separate file
  - ▶ module header comment segment with a basic functional description
  - ▶ I/O ports description
  - ▶ utilise parameters or definitions
    - ▶ *parameter* vs *`define*
  - ▶ for each instantiation/implementation add header comment
    - ▶ describe explicit corner cases
- ▶ Follow a uniform coding style across all files
  - ▶ comments
  - ▶ indentations
  - ▶ `begin-end` usage and format
  - ▶ *etc.*

# Overview

---

- ▶ Fundamental Acquired Skills after Completing Lab Assignment 1
  - ▶ Dataflow & Top-level Module (*Golden Rule #1*)
  - ▶ Combinational vs Sequential always blocks (*Golden Rule #2*)
    - ▶ Minimal Implementation with Sequential Elements
  - ▶ Reset & Clock Logic (*Golden Rule #4*)
- ▶ Review Implementation Faults
  - ▶ Hierarchical Design, Coding Style & Comments
  - ▶ **Combinational Logic Reset**
  - ▶ Anode Driver Refresh Period
  - ▶ Debouncer
  - ▶ MMCM Reset
  - ▶ MMCM Feedback
  - ▶ MMCM VCO Minimum Frequency
  - ▶ Registers' Memory vs FPGA ROM
  - ▶ XDC Constraints Usage & Justification
- ▶ Fundamental Acquired Skills after Completing Lab Assignment 2
  - ▶ FSMs
  - ▶ Testbench
  - ▶ Satisfy Timing Requirements

# Combinational Logic & Reset

- ▶ Does combinational logic require reset logic?
  - ▶ as described below:

```
always @(signal_1 or ... or signal_x)
begin
    if (reset)
    begin
        signal_1 = 1'b0;
        ...
        signal_x = 1'b1;
    end // if (reset) //
else
    begin
        ...
    end // else //
end // always @(signal_1 or ... or signal_x) //
```

# Correct Implementation of reset in combinational blocks



```
1  always @(signal_1 or signal_2)
2  begin
3      if(enable == 1'b0)
4      begin
5          signal_1 = 1'b0;
6          signal_2 = 1'b0;
7      end
8      else
9      begin
10         ....
11     end
12 end
```



```
1  always @(posedge clk or posedge reset)
2  begin
3      if(reset == 1'b1)
4      begin
5          enable <= 1'b0;
6      end
7      else
8      begin
9          enable <= 1'b1;
10     end
11 end
```

# Overview

---

- ▶ Fundamental Acquired Skills after Completing Lab Assignment 1
  - ▶ Dataflow & Top-level Module (*Golden Rule #1*)
  - ▶ Combinational vs Sequential always blocks (*Golden Rule #2*)
    - ▶ Minimal Implementation with Sequential Elements
  - ▶ Reset & Clock Logic (*Golden Rule #4*)
- ▶ Review Implementation Faults
  - ▶ Hierarchical Design, Coding Style & Comments
  - ▶ Combinational Logic Reset
  - ▶ **Anode Driver Refresh Period**
  - ▶ Debouncer
  - ▶ MMCM Reset
  - ▶ MMCM Feedback
  - ▶ MMCM VCO Minimum Frequency
  - ▶ Registers' Memory vs FPGA ROM
  - ▶ XDC Constraints Usage & Justification
- ▶ Fundamental Acquired Skills after Completing Lab Assignment 2
  - ▶ FSMs
  - ▶ Testbench
  - ▶ Satisfy Timing Requirements

# Anode Driver Refresh Period

## ► 9.1 Seven-Segment Display - Nexys A7 Reference Manual

To illuminate a segment, the anode should be driven high while the cathode is driven low. However, since the Nexys A7 uses transistors to drive enough current into the common anode point, the anode enables are inverted. Therefore, both the AN0..7 and the CA..G/DP signals are driven low when active.

 


Figure 9.1.2 Common Anode Circuit Node

For each of the four digits to appear bright and continuously illuminated, all eight digits should be driven once every 1 to 16ms, for a refresh frequency of about 1 KHz to 60Hz. For example, in a 62.5Hz refresh scheme, the entire display would be refreshed once every 16ms, and each digit would be illuminated for 1/8 of the refresh cycle, or 2ms. The controller must drive low the cathodes with the correct pattern when the corresponding anode signal is driven high. To illustrate the process, if


 


Figure 9.1.3 Four Digit Scanning Display Controller Timing Diagram

# Anode Driver Refresh Period
 
## ► 9.1 Seven-Segment Display - Nexys A7 Reference Manual

To illuminate a segment, the anode should be driven high while the cathode is driven low. However, since the Nexys A7 uses transistors to drive enough current into the common anode point, the anode enables are inverted. Therefore, both the AN0..7 and the CA..G/DP signals are driven low when a



Everything you need to know, especially for provided Xilinx/Digilent IPs and functionality, is documented in related manuals

Figure 9.1.2 Common Anode Circuit Node

For each of the four digits to appear bright and continuously illuminated, all eight digits should be driven once every 1 to 16ms, for a refresh frequency of about 1 KHz to 60Hz. For example, in a 62.5Hz refresh scheme, the entire display would be refreshed once every 16ms, and each digit would be illuminated for 1/8 of the refresh cycle, or 2ms. The controller must drive low the cathodes with the correct pattern when the corresponding anode signal is driven high. To illustrate the process, if

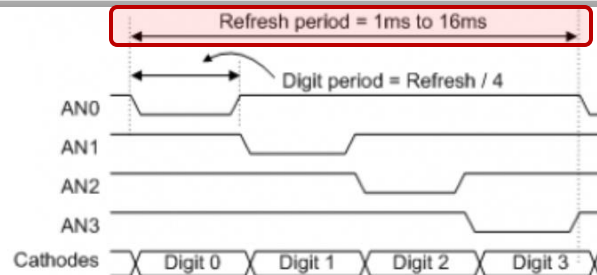


Figure 9.1.3 Four Digit Scanning Display Controller Timing Diagram



# Overview

---

- ▶ Fundamental Acquired Skills after Completing Lab Assignment 1
  - ▶ Dataflow & Top-level Module (*Golden Rule #1*)
  - ▶ Combinational vs Sequential always blocks (*Golden Rule #2*)
    - ▶ Minimal Implementation with Sequential Elements
  - ▶ Reset & Clock Logic (*Golden Rule #4*)
- ▶ Review Implementation Faults
  - ▶ Hierarchical Design, Coding Style & Comments
  - ▶ Combinational Logic Reset
  - ▶ Anode Driver Refresh Period
  - ▶ Debouncer
  - ▶ MMCM Reset
  - ▶ MMCM Feedback
  - ▶ MMCM VCO Minimum Frequency
  - ▶ Registers' Memory vs FPGA ROM
  - ▶ XDC Constraints Usage & Justification
- ▶ Fundamental Acquired Skills after Completing Lab Assignment 2
  - ▶ FSMs
  - ▶ Testbench
  - ▶ Satisfy Timing Requirements

# Debouncer & Reset Signal

- ▶ How can you simultaneously
  - ▶ count bouncing glitches, and
  - ▶ reset utilised counter & synchroniser flip-flop(s)
- ▶ using the same signal?

```
// 2 Stage Pipeline Synchroniser with Asynchronous Reset //
always @(posedge clock or posedge reset)
begin
    if (reset)
    begin
        sync_pipe_stage1 <= 1'b1;
        reset_sync <= 1'b1;
    end // if (reset) //
    else
    begin
        sync_pipe_stage1 <= reset;
        reset_sync <= sync_pipe_stage1;
    end // else //
end // always @(posedge clock or posedge reset) //
```

# Debouncer & Reset Signal

- ▶ How can you simultaneously
  - ▶ count bouncing glitches, and
  - ▶ reset utilised counter & synchroniser flip-flop(s)
- ▶ using the same signal?

```
// 2 Stage Pipeline Synchroniser with Asynchronous Reset //
always @(posedge clock or posedge reset)
begin
    if (reset)
    begin
        sync_pipe_stagel = 1'b1;
        reset_sync = 1'b1;
    end // if (reset) //
    else
    begin
        sync_pipe_stagel <= reset;
        reset_sync <= sync_pipe_stagel;
    end // else //
end // always @(posedge clock or posedge reset) //
```

# Debouncer & Logic Comparison in Time

- ▶ What is the duration of bouncing effect for a button on FPGA?
  - ▶ about  $\approx 5\text{-}10\text{ms}$ 
    - ▶ determined after a **5min** search on the internet
- ▶ How do we compare logic signals ( $=$  or  $\neq$ )?

**XOR**

X	Y	$X \oplus Y$
0	0	0
0	1	1
1	0	1
1	1	0


XOR Symbol




**XNOR**

X	Y	$\overline{X \oplus Y}$
0	0	1
0	1	0
1	0	0
1	1	1

XNOR Symbol

 

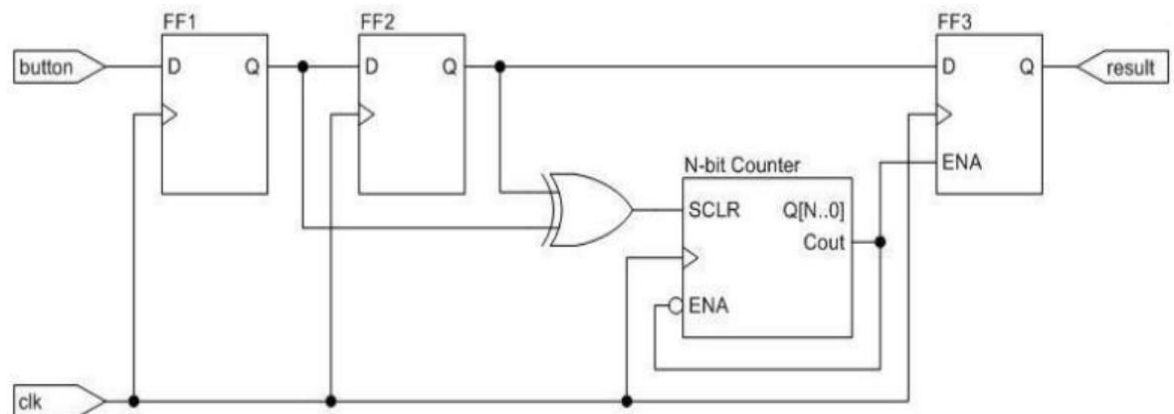- The XNOR is also denoted as **equivalence**



- ▶ *some useful sources:*

- ▶ [11 Myths about Switch Bounce/Debounce | www.electronicdesign.com](http://www.electronicdesign.com)
- ▶ [Switch Debounce Using TMR2 | microchipdeveloper.com](http://microchipdeveloper.com)

# Overview

---

- ▶ Fundamental Acquired Skills after Completing Lab Assignment 1
  - ▶ Dataflow & Top-level Module (*Golden Rule #1*)
  - ▶ Combinational vs Sequential always blocks (*Golden Rule #2*)
    - ▶ Minimal Implementation with Sequential Elements
  - ▶ Reset & Clock Logic (*Golden Rule #4*)
- ▶ Review Implementation Faults
  - ▶ Hierarchical Design, Coding Style & Comments
  - ▶ Combinational Logic Reset
  - ▶ Anode Driver Refresh Period
  - ▶ Debouncer
  - ▶ **MMCM Reset**
  - ▶ MMCM Feedback
  - ▶ MMCM VCO Minimum Frequency
  - ▶ Registers' Memory vs FPGA ROM
  - ▶ XDC Constraints Usage & Justification
- ▶ Fundamental Acquired Skills after Completing Lab Assignment 2
  - ▶ FSMs
  - ▶ Testbench
  - ▶ Satisfy Timing Requirements

# MMCM Reset

## ▶ LOCKED - Status and Data Outputs

### ▶ 7 Series FPGAs Clocking Resources - User Guide

#### LOCKED

An output from the MMCM/PLL used to indicate when the MMCM/PLL have achieved phase and frequency alignment of the reference clock and the feedback clock at the input pins. Phase alignment is within a predefined window and frequency matching within a predefined PPM range. The MMCM automatically locks after power on, no extra reset is required. LOCKED will be deasserted within one PFD clock cycle if the input clock stops, the phase alignment is violated (for example, input clock phase shift) or the frequency has changed. The MMCM/PLL must be reset when LOCKED is deasserted. The clock outputs should not be used prior to the assertion of LOCKED.

▶ What is the purpose of LOCKED signal?

# MMCM Reset

## ▶ LOCKED - Status and Data Outputs

### ▶ 7 Series FPGAs Clocking Resources - User Guide

#### LOCKED

An output from the MMCM/PLL used to indicate when the MMCM/PLL have achieved phase and frequency alignment of the reference clock and the feedback clock at the input pins. Phase alignment is within a predefined window and frequency matching within a predefined PPM range. The MMCM automatically locks after power on, no extra reset is required. LOCKED will be deasserted within one PFD clock cycle if the input clock stops, the phase alignment is violated (for example, input clock phase shift) or the frequency has changed. The MMCM/PLL must be reset when LOCKED is deasserted. **The clock outputs should not be used prior to the assertion of LOCKED.**

## ▶ If you used the synchronised-debounced reset for MMCM

### ▶ you should consider LOCKED signal

#### ▶ as a **reset?**

□ or

#### ▶ as a **clock enable?**

□ *for the rest of your design*

# MMCM Reset

## ▶ LOCKED - Status and Data Outputs

### ▶ 7 Series FPGAs Clocking Resources - User Guide

#### LOCKED

An output from the MMCM/PLL used to indicate when the MMCM/PLL have achieved phase and frequency alignment of the reference clock and the feedback clock at the input pins. Phase alignment is within a predefined window and frequency matching within a predefined PPM range. The MMCM automatically locks after power on, no extra reset is required. LOCKED will be deasserted within one PFD clock cycle if the input clock stops, the phase alignment is violated (for example, input clock phase shift) or the frequency has changed. The MMCM/PLL must be reset when LOCKED is deasserted. **The clock outputs should not be used prior to the assertion of LOCKED.**

## ▶ If you used the synchronised-debounced reset for MMCM

### ▶ you should consider LOCKED signal

▶ as **a reset**

□ or

▶ as **a clock enable**

□ *for the rest of your design*

For the purposes of this course, you **must follow Golden Rule #4.**

When you become advanced designers, *you may consider the implementation as reset logic.*



# Overview

---

- ▶ Fundamental Acquired Skills after Completing Lab Assignment 1
  - ▶ Dataflow & Top-level Module (*Golden Rule #1*)
  - ▶ Combinational vs Sequential always blocks (*Golden Rule #2*)
    - ▶ Minimal Implementation with Sequential Elements
  - ▶ Reset & Clock Logic (*Golden Rule #4*)
- ▶ Review Implementation Faults
  - ▶ Hierarchical Design, Coding Style & Comments
  - ▶ Combinational Logic Reset
  - ▶ Anode Driver Refresh Period
  - ▶ Debouncer
  - ▶ MMCM Reset
  - ▶ **MMCM Feedback**
  - ▶ MMCM VCO Minimum Frequency
  - ▶ Registers' Memory vs FPGA ROM
  - ▶ XDC Constraints Usage & Justification
- ▶ Fundamental Acquired Skills after Completing Lab Assignment 2
  - ▶ FSMs
  - ▶ Testbench
  - ▶ Satisfy Timing Requirements

# MMCM Feedback

## ▶ CLKFBIN - Feedback Clock Input

### ▶ 7 Series FPGAs Clocking Resources - User Guide

#### CLKFBIN – Feedback Clock Input

Must be connected either directly to the CLKFBOUT for internal feedback or IBUFG (through a clock-capable pin for external deskew), BUFG, BUFGH, or interconnect (not recommended). For external clock alignment, the feedback path clock buffer type should match the forward clock buffer type with the exception of BUFR. BUFR cannot be compensated for.

# MMCM Feedback

## ▶ CLKFBIN - Feedback Clock Input

### ▶ 7 Series FPGAs Clocking Resources - User Guide

#### CLKFBIN – Feedback Clock Input

Must be connected either directly to the CLKFBOUT for internal feedback or IBUFG (through a clock-capable pin for external deskew), BUFG, BUFGH, or interconnect (not recommended). For external clock alignment, the feedback path clock buffer type should match the forward clock buffer type with the exception of BUFR. BUFR cannot be compensated for.

Everything you need to know,  
**especially for provided  
Xilinx/Digilent IPs and  
functionality**, is documented in  
related manuals

# Overview

---

- ▶ Fundamental Acquired Skills after Completing Lab Assignment 1
  - ▶ Dataflow & Top-level Module (*Golden Rule #1*)
  - ▶ Combinational vs Sequential always blocks (*Golden Rule #2*)
    - ▶ Minimal Implementation with Sequential Elements
  - ▶ Reset & Clock Logic (*Golden Rule #4*)
- ▶ Review Implementation Faults
  - ▶ Hierarchical Design, Coding Style & Comments
  - ▶ Combinational Logic Reset
  - ▶ Anode Driver Refresh Period
  - ▶ Debouncer
  - ▶ MMCM Reset
  - ▶ MMCM Feedback
  - ▶ **MMCM VCO Minimum Frequency**
  - ▶ Registers' Memory vs FPGA ROM
  - ▶ XDC Constraints Usage & Justification
- ▶ Fundamental Acquired Skills after Completing Lab Assignment 2
  - ▶ FSMs
  - ▶ Testbench
  - ▶ Satisfy Timing Requirements

# MMCM VCO Minimum Frequency

## ▶ Voltage-Controlled Oscillator (VCO)

- ▶ VCO operates @600MHz by default, meaning
  - ▶ for default parameters, and
  - ▶ system clock @100MHz as input clock
- ▶ Thus, all provided output clocks operate @600MHz
  - ▶ with default parameters

$$F_{VCO} = F_{CLKIN} \times \frac{M}{D}$$

$$F_{OUT} = F_{CLKIN} \times \frac{M}{D \times O}$$

**Which is the  
minimum achievable  
frequency?**

**Did you consider  
VCO frequency?  
OR  
System Clock's frequency?**

# Overview

---

- ▶ Fundamental Acquired Skills after Completing Lab Assignment 1
  - ▶ Dataflow & Top-level Module (*Golden Rule #1*)
  - ▶ Combinational vs Sequential always blocks (*Golden Rule #2*)
    - ▶ Minimal Implementation with Sequential Elements
  - ▶ Reset & Clock Logic (*Golden Rule #4*)
- ▶ Review Implementation Faults
  - ▶ Hierarchical Design, Coding Style & Comments
  - ▶ Combinational Logic Reset
  - ▶ Anode Driver Refresh Period
  - ▶ Debouncer
  - ▶ MMCM Reset
  - ▶ MMCM Feedback
  - ▶ MMCM VCO Minimum Frequency
  - ▶ **Registers' Memory vs FPGA ROM**
  - ▶ XDC Constraints Usage & Justification
- ▶ Fundamental Acquired Skills after Completing Lab Assignment 2
  - ▶ FSMs
  - ▶ Testbench
  - ▶ Satisfy Timing Requirements

# Registers' Memory vs FPGA ROM

```
reg [3:0] message [0:15];
```

- ▶ Delivered code for required memory
  - ▶ Which are correct?

```
assign message[0] = CHAR_0;
assign message[1] = CHAR_1;
assign message[2] = CHAR_2;
assign message[3] = CHAR_3;
assign message[4] = CHAR_4;
assign message[5] = CHAR_5;
assign message[6] = CHAR_6;
assign message[7] = CHAR_7;
assign message[8] = CHAR_8;
assign message[9] = CHAR_9;
assign message[10] = CHAR_A;
assign message[11] = CHAR_B;
assign message[12] = CHAR_C;
assign message[13] = CHAR_D;
assign message[14] = CHAR_E;
assign message[15] = CHAR_F;

assign char = message[address];
```

```
always @(posedge clk)
begin
    if (reset)
        begin
            message[0] = CHAR_0;
            message[1] = CHAR_1;
            message[2] = CHAR_2;
            message[3] = CHAR_3;
            message[4] = CHAR_4;
            message[5] = CHAR_5;
            message[6] = CHAR_6;
            message[7] = CHAR_7;
            message[8] = CHAR_8;
            message[9] = CHAR_9;
            message[10] = CHAR_A;
            message[11] = CHAR_B;
            message[12] = CHAR_C;
            message[13] = CHAR_D;
            message[14] = CHAR_E;
            message[15] = CHAR_F;
        end
end

always @(posedge clk)
begin
    if (reset == 1'b0)
        char <= 4'd0;
    else
        char <= message[address];
end

assign char = message[address];
```

```
always @(posedge clk or posedge reset)
begin
    if (reset)
        begin
            message[0] = CHAR_0;
            message[1] = CHAR_1;
            message[2] = CHAR_2;
            message[3] = CHAR_3;
            message[4] = CHAR_4;
            message[5] = CHAR_5;
            message[6] = CHAR_6;
            message[7] = CHAR_7;
            message[8] = CHAR_8;
            message[9] = CHAR_9;
            message[10] = CHAR_A;
            message[11] = CHAR_B;
            message[12] = CHAR_C;
            message[13] = CHAR_D;
            message[14] = CHAR_E;
            message[15] = CHAR_F;
        end
end

always @(posedge clk or posedge reset)
begin
    if (reset)
        begin
            message[0] <= CHAR_0;
            message[1] <= CHAR_1;
            message[2] <= CHAR_2;
            message[3] <= CHAR_3;
            message[4] <= CHAR_4;
            message[5] <= CHAR_5;
            message[6] <= CHAR_6;
            message[7] <= CHAR_7;
            message[8] <= CHAR_8;
            message[9] <= CHAR_9;
            message[10] <= CHAR_A;
            message[11] <= CHAR_B;
            message[12] <= CHAR_C;
            message[13] <= CHAR_D;
            message[14] <= CHAR_E;
            message[15] <= CHAR_F;
        end
    else
        begin
            char <= message[address];
        end
end

assign char = message[address];
```

```
initial
begin
    message[0] = CHAR_0;
    message[1] = CHAR_1;
    message[2] = CHAR_2;
    message[3] = CHAR_3;
    message[4] = CHAR_4;
    message[5] = CHAR_5;
    message[6] = CHAR_6;
    message[7] = CHAR_7;
    message[8] = CHAR_8;
    message[9] = CHAR_9;
    message[10] = CHAR_A;
    message[11] = CHAR_B;
    message[12] = CHAR_C;
    message[13] = CHAR_D;
    message[14] = CHAR_E;
    message[15] = CHAR_F;
end

always @(posedge clk)
begin
    if (reset == 1'b0)
        char <= 4'd0;
    else
        char <= message[address];
end

assign char = message[address];
```

# Registers' Memory vs FPGA ROM

```
reg [3:0] message [0:15];
```

- ▶ Delivered code for required memory
  - ▶ Which are correct?

The diagram illustrates six different Verilog code snippets for initializing and accessing a 16-bit memory array named `message`. Each snippet is evaluated for correctness based on standard Verilog practices for memory initialization and access.

- Snippet 1 (Leftmost):** Uses a series of `assign` statements to initialize each element of the `message` array. This is a non-standard and inefficient way to initialize memory in Verilog. **Incorrect (marked with a red X).**
- Snippet 2:** Uses an `always` block with a `posedge clk` trigger to initialize the `message` array. This is also non-standard. **Incorrect (marked with a red X).**
- Snippet 3:** Uses an `always` block with a `posedge clk or posedge reset` trigger to initialize the `message` array. This is a standard and correct way to initialize memory in Verilog. **Correct (marked with a yellow checkmark).**
- Snippet 4:** Uses an `always` block with a `posedge clk or posedge reset` trigger to initialize the `message` array. This is a standard and correct way to initialize memory in Verilog. **Correct (marked with a yellow checkmark).**
- Snippet 5:** Uses an `always` block with a `posedge clk or posedge reset` trigger to initialize the `message` array. This is a standard and correct way to initialize memory in Verilog. **Correct (marked with a yellow checkmark).**
- Snippet 6 (Rightmost):** Uses an `initial` block to initialize the `message` array. This is a standard and correct way to initialize memory in Verilog. **Correct (marked with a yellow checkmark).**

Below the snippets, there are two more code blocks:

- Snippet 7:** An `always` block with a `posedge clk` trigger that updates the `char` register based on the `message` array. This is a standard and correct way to access memory in Verilog. **Correct (marked with a yellow checkmark).**
- Snippet 8:** An `always` block with a `posedge clk` trigger that updates the `char` register based on the `message` array. This is a standard and correct way to access memory in Verilog. **Correct (marked with a yellow checkmark).**

At the bottom right, there is a final code block:


```
assign char = message[address];
```


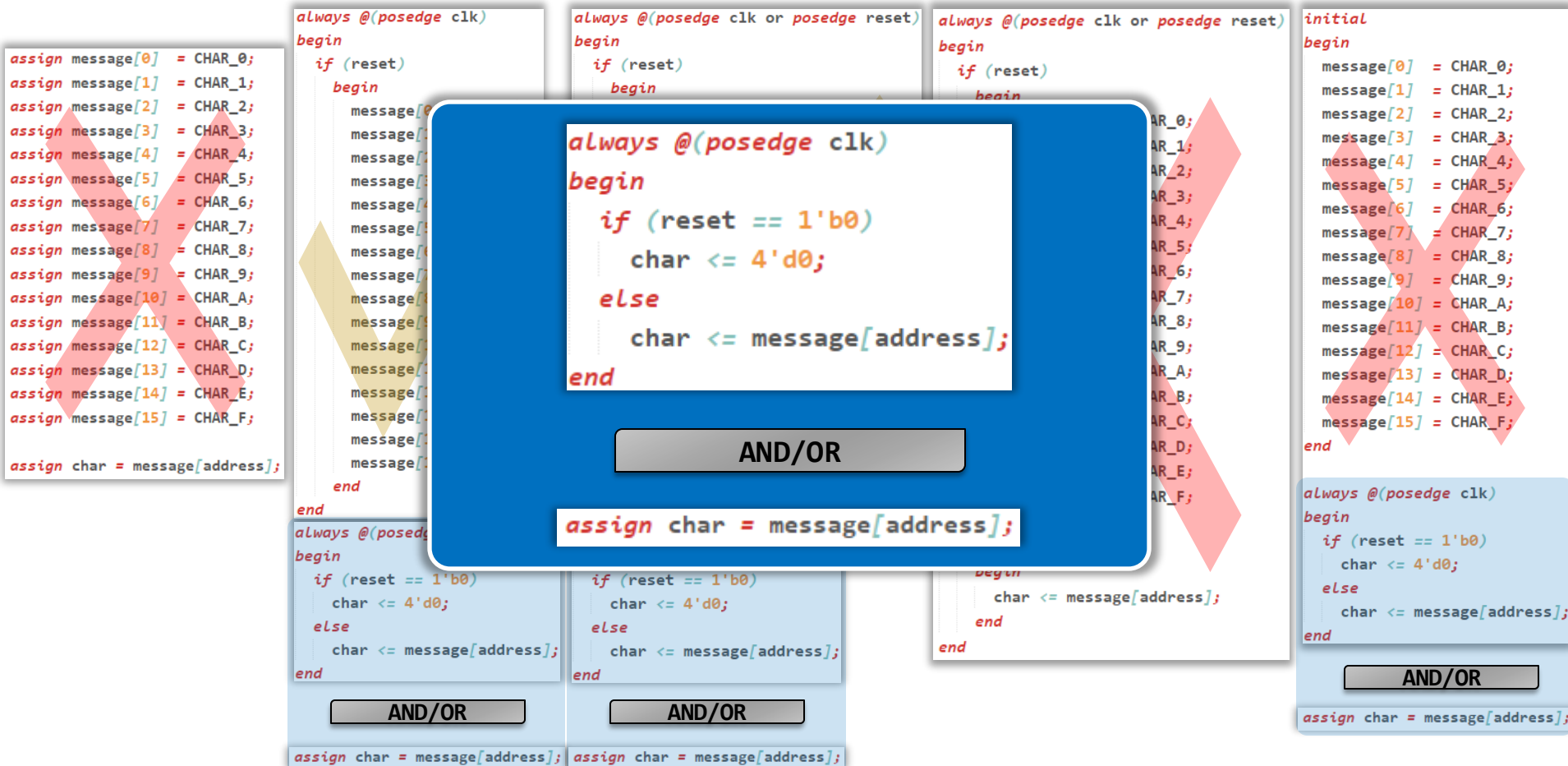
# Registers' Memory vs FPGA ROM

```
reg [3:0] message [0:15];
```


- ▶ Delivered code for required memory
  - ▶ Which are correct?


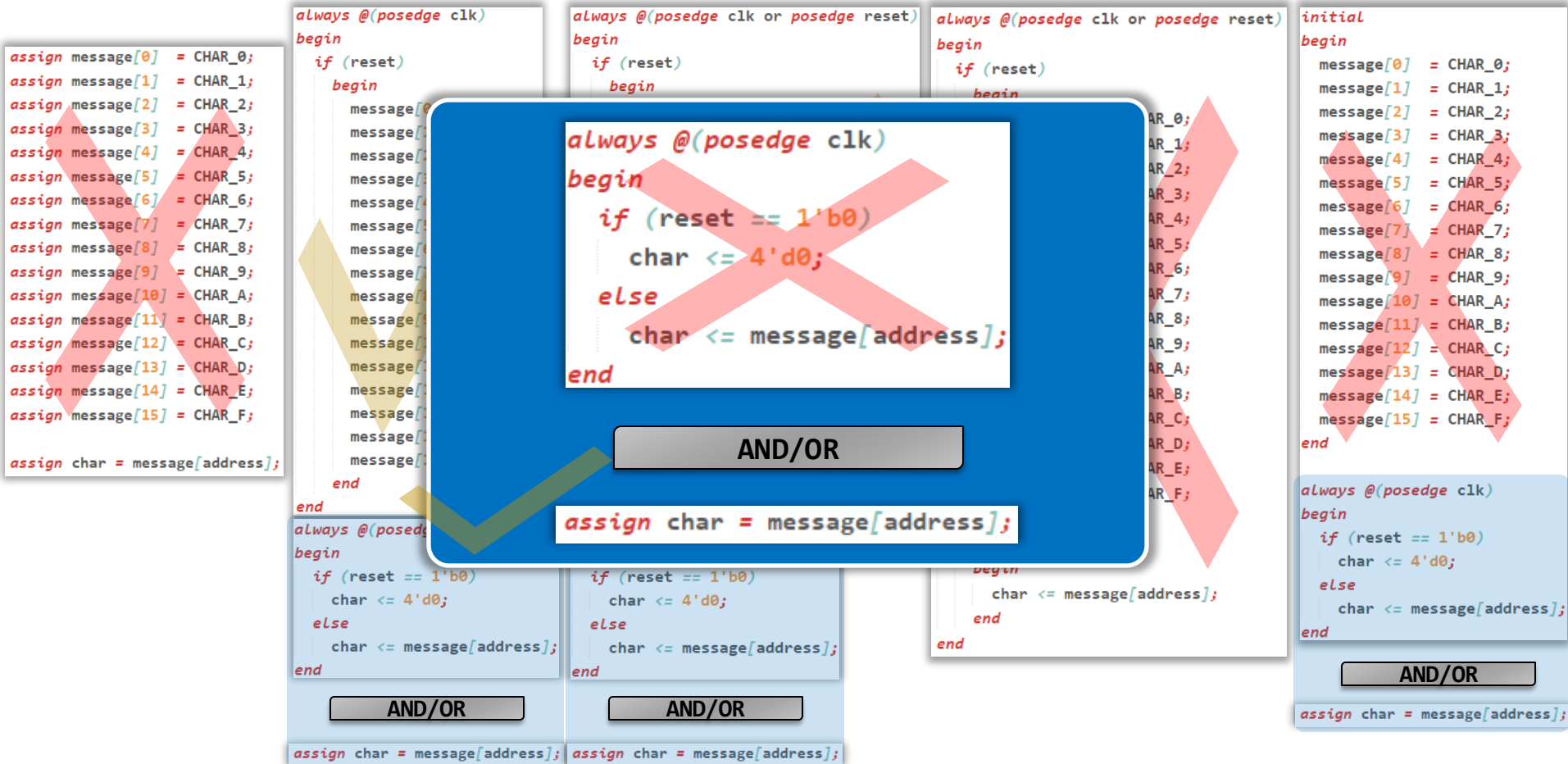
# Registers' Memory vs FPGA ROM

```
reg [3:0] message [0:15];
```

- ▶ Delivered code for required memory
  - ▶ Which are correct?



# Registers' Memory vs FPGA ROM

```
reg [3:0] message [0:15];
```

- ▶ Delivered code for required memory
  - ▶ Which are correct?

The image displays several Verilog code snippets for initializing a 16-element register array named `message`. The snippets are arranged in a grid, with most being crossed out by a large red 'X' to indicate they are incorrect. The correct snippets are highlighted with yellow arrows.

**Incorrect snippets (crossed out):**

- `assign message[0] = CHAR_0; assign message[1] = CHAR_1; assign message[2] = CHAR_2; assign message[3] = CHAR_3; assign message[4] = CHAR_4; assign message[5] = CHAR_5; assign message[6] = CHAR_6; assign message[7] = CHAR_7; assign message[8] = CHAR_8; assign message[9] = CHAR_9; assign message[10] = CHAR_A; assign message[11] = CHAR_B; assign message[12] = CHAR_C; assign message[13] = CHAR_D; assign message[14] = CHAR_E; assign message[15] = CHAR_F; assign char = message[address];`
- `always @(posedge clk) begin if (reset) begin message[0] = CHAR_0; message[1] = CHAR_1; message[2] = CHAR_2; message[3] = CHAR_3; message[4] = CHAR_4; message[5] = CHAR_5; message[6] = CHAR_6; message[7] = CHAR_7; message[8] = CHAR_8; message[9] = CHAR_9; message[10] = CHAR_A; message[11] = CHAR_B; message[12] = CHAR_C; message[13] = CHAR_D; message[14] = CHAR_E; message[15] = CHAR_F; end end`
- `always @(posedge clk or posedge reset) begin if (reset) begin message[0] = CHAR_0; message[1] = CHAR_1; message[2] = CHAR_2; message[3] = CHAR_3; message[4] = CHAR_4; message[5] = CHAR_5; message[6] = CHAR_6; message[7] = CHAR_7; message[8] = CHAR_8; message[9] = CHAR_9; message[10] = CHAR_A; message[11] = CHAR_B; message[12] = CHAR_C; message[13] = CHAR_D; message[14] = CHAR_E; message[15] = CHAR_F; end end`
- `always @(posedge clk or posedge reset) begin if (reset) begin message[0] <= CHAR_0; message[1] <= CHAR_1; message[2] <= CHAR_2; message[3] <= CHAR_3; message[4] <= CHAR_4; message[5] <= CHAR_5; message[6] <= CHAR_6; message[7] <= CHAR_7; message[8] <= CHAR_8; message[9] <= CHAR_9; message[10] <= CHAR_A; message[11] <= CHAR_B; message[12] <= CHAR_C; message[13] <= CHAR_D; message[14] <= CHAR_E; message[15] <= CHAR_F; end else begin char <= message[address]; end end`
- `initial begin message[0] = CHAR_0; message[1] = CHAR_1; message[2] = CHAR_2; message[3] = CHAR_3; message[4] = CHAR_4; message[5] = CHAR_5; message[6] = CHAR_6; message[7] = CHAR_7; message[8] = CHAR_8; message[9] = CHAR_9; message[10] = CHAR_A; message[11] = CHAR_B; message[12] = CHAR_C; message[13] = CHAR_D; message[14] = CHAR_E; message[15] = CHAR_F; end`
- `always @(posedge clk) begin if (reset == 1'b0) char <= 4'd0; else char <= message[address]; end`
- `always @(posedge clk) begin if (reset == 1'b0) char <= 4'd0; else char <= message[address]; end`

**Correct snippets (highlighted with yellow arrows):**

- `always @(posedge clk) begin if (reset) begin message[0] = CHAR_0; message[1] = CHAR_1; message[2] = CHAR_2; message[3] = CHAR_3; message[4] = CHAR_4; message[5] = CHAR_5; message[6] = CHAR_6; message[7] = CHAR_7; message[8] = CHAR_8; message[9] = CHAR_9; message[10] = CHAR_A; message[11] = CHAR_B; message[12] = CHAR_C; message[13] = CHAR_D; message[14] = CHAR_E; message[15] = CHAR_F; end end`
- `assign char = message[address];`

# Memory/Register Initialisation

```
▶ reg [3:0] message [0:15];
```

We can use an *initial* block only for registers & some ROMs/RAMs only in FPGA design, but it is NOT ASIC-proven.

Basically, we **JUST** define *their initial value when the core turns on*.

```
initial
begin
    message[0] = CHAR_0;
    message[1] = CHAR_1;
    message[2] = CHAR_2;
    message[3] = CHAR_3;
    message[4] = CHAR_4;
    message[5] = CHAR_5;
    message[6] = CHAR_6;
    message[7] = CHAR_7;
    message[8] = CHAR_8;
    message[9] = CHAR_9;
    message[10] = CHAR_A;
    message[11] = CHAR_B;
    message[12] = CHAR_C;
    message[13] = CHAR_D;
    message[14] = CHAR_E;
    message[15] = CHAR_F;
end
```

# Overview

---

- ▶ Fundamental Acquired Skills after Completing Lab Assignment 1
  - ▶ Dataflow & Top-level Module (*Golden Rule #1*)
  - ▶ Combinational vs Sequential always blocks (*Golden Rule #2*)
    - ▶ Minimal Implementation with Sequential Elements
  - ▶ Reset & Clock Logic (*Golden Rule #4*)
- ▶ Review Implementation Faults
  - ▶ Hierarchical Design, Coding Style & Comments
  - ▶ Combinational Logic Reset
  - ▶ Anode Driver Refresh Period
  - ▶ Debouncer
  - ▶ MMCM Reset
  - ▶ MMCM Feedback
  - ▶ MMCM VCO Minimum Frequency
  - ▶ Registers' Memory vs FPGA ROM
  - ▶ XDC Constraints Usage & Justification
- ▶ Fundamental Acquired Skills after Completing Lab Assignment 2
  - ▶ FSMs
  - ▶ Testbench
  - ▶ Satisfy Timing Requirements

# XDC Constrains Usage & Justification

## ▶ Warning-Free vs Ignoring Warning(s)

- ▶ you have to justify both
- ▶ both choices are equally important
  - ▶ Meaning we expect from you to resolve upcoming issues

□ with **Critical Thinking**



## ▶ So, whenever you ignore or add/implement something,

- ▶ You should be able to explain
  - ▶ *Why?*
  - ▶ *How it works?*
    - i.e., `VOLTAGE_CONFIG`

# Wrong Initialisation on variables

```
module test_counter(clk, reset, count)
    input clk, reset;
    output [3:0] count;
    reg [3:0] count;

    wire enable = 1'b1;
    reg var_1 = 1'b1;
```

It is **not valid** to initialise registers and wires like this!

It is not like C that we can set initial values on variables!

```
module test_counter(clk, reset, count)
    input clk, reset;
    output [3:0] count;
    reg [3:0] count;

    wire enable;
    reg var_1;

    always @(posedge clk or posedge reset)
    begin
        if (reset)
        begin
            var_1 <= 1'b1;
            count <= 4'b0000;
        end
        else
            count <= count + 1'b1;
        end
    end

    always @(var_1)
    begin
        if (var_1)
            enable = 1'b1;
        else
            enable = 1'b0;
        end
    end
```

**All registers should get initial value on reset!**

**All wires should get value according to register's value**

# Overview

---

- ▶ Fundamental Acquired Skills after Completing Lab Assignment 1
  - ▶ Dataflow & Top-level Module (*Golden Rule #1*)
  - ▶ Combinational vs Sequential always blocks (*Golden Rule #2*)
    - ▶ Minimal Implementation with Sequential Elements
  - ▶ Reset & Clock Logic (*Golden Rule #4*)
- ▶ Review Implementation Faults
  - ▶ Hierarchical Design, Coding Style & Comments
  - ▶ Combinational Logic Reset
  - ▶ Anode Driver Refresh Period
  - ▶ Debouncer
  - ▶ MMCM Reset
  - ▶ MMCM Feedback
  - ▶ MMCM VCO Minimum Frequency
  - ▶ Registers' Memory vs FPGA ROM
  - ▶ XDC Constraints Usage & Justification
- ▶ Fundamental Acquired Skills after Completing Lab Assignment 2
  - ▶ FSMs
  - ▶ Testbench
  - ▶ Satisfy Timing Requirements



# Questions

---

