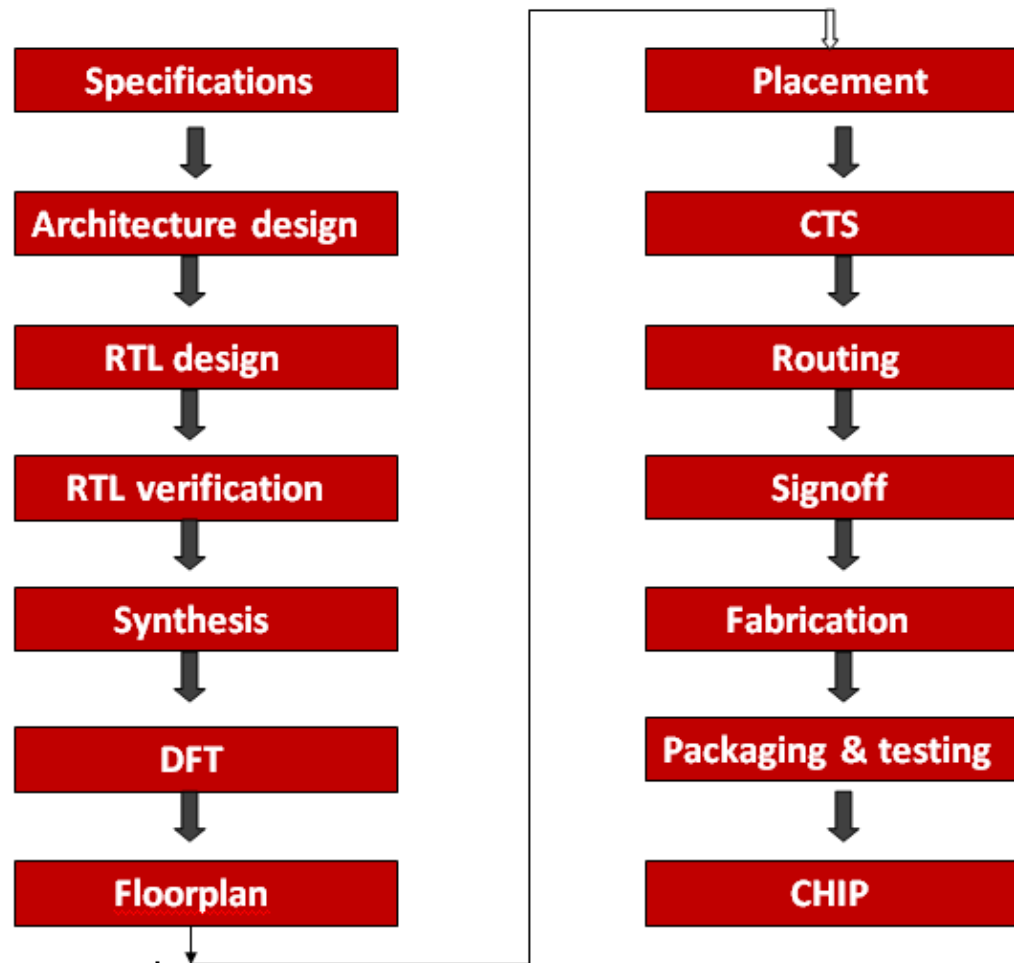



CE327 - Digital VLSI Systems Semester Project Presentation Fall Semester - 2022

I. Lilitsis, I. Gkolfos, S. Simoglou, C. Sotiriou


ASIC Design Flow




ASIC Design Flow

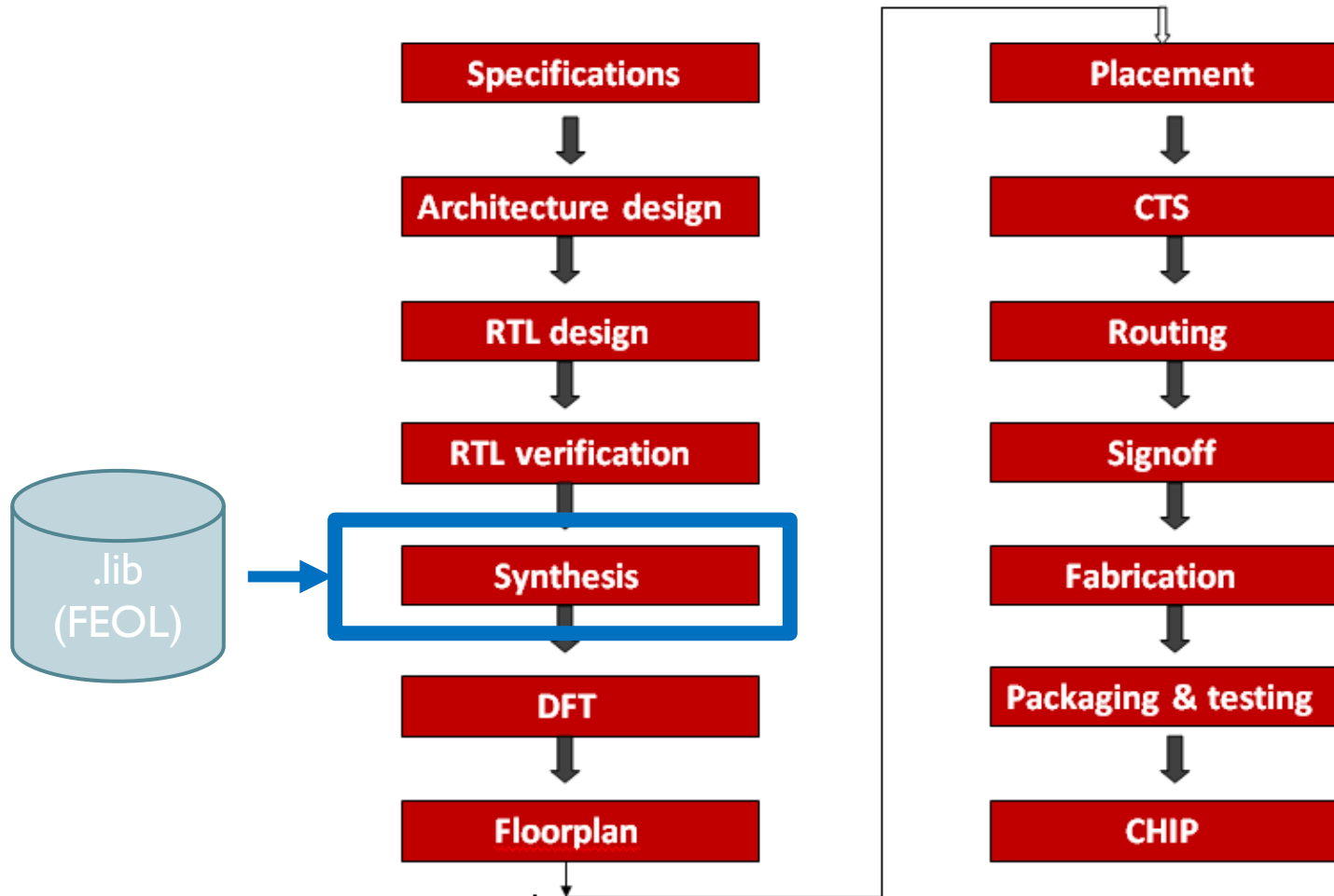

ASIC Design Flow

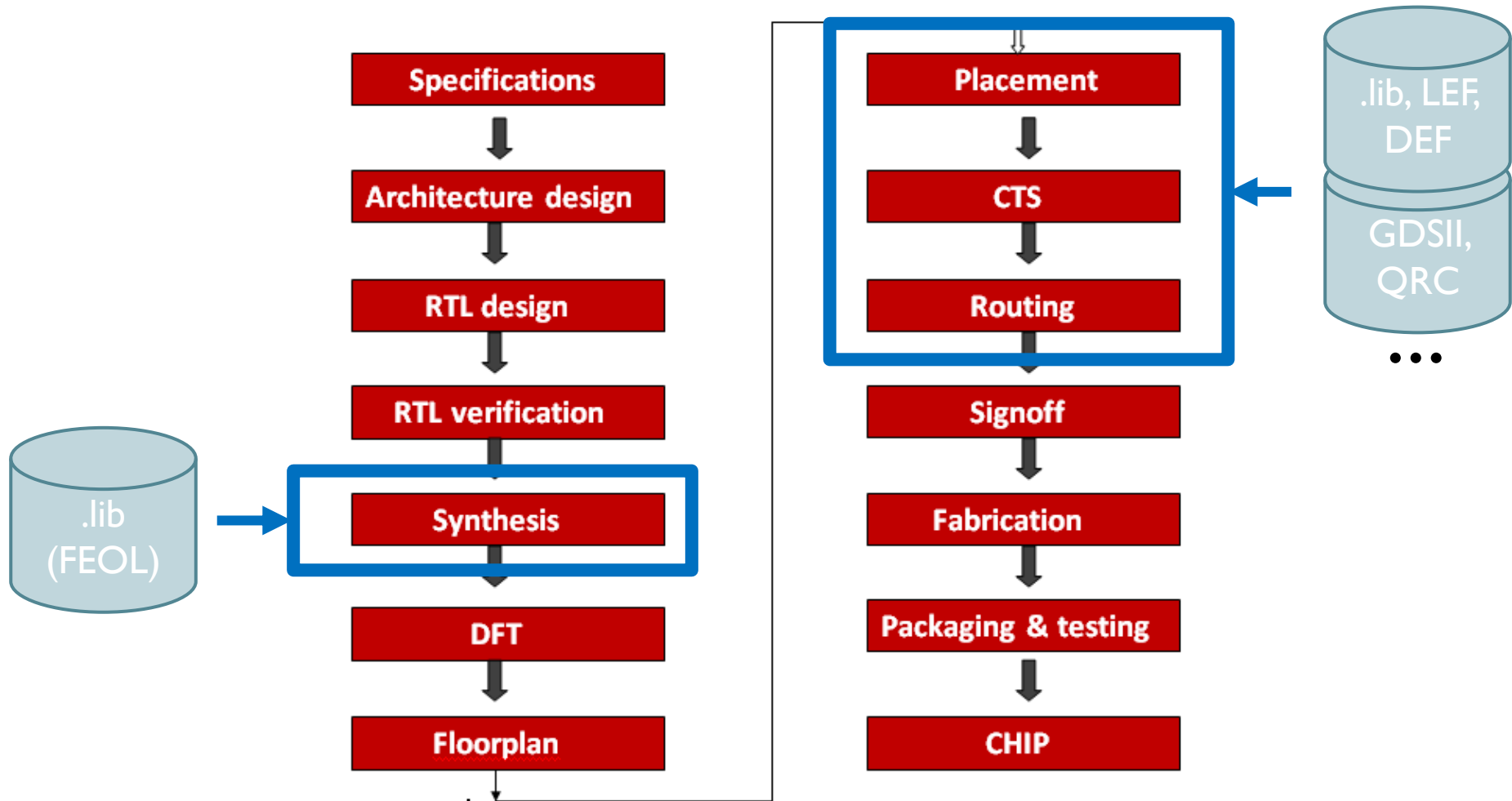


ASIC Design Flow

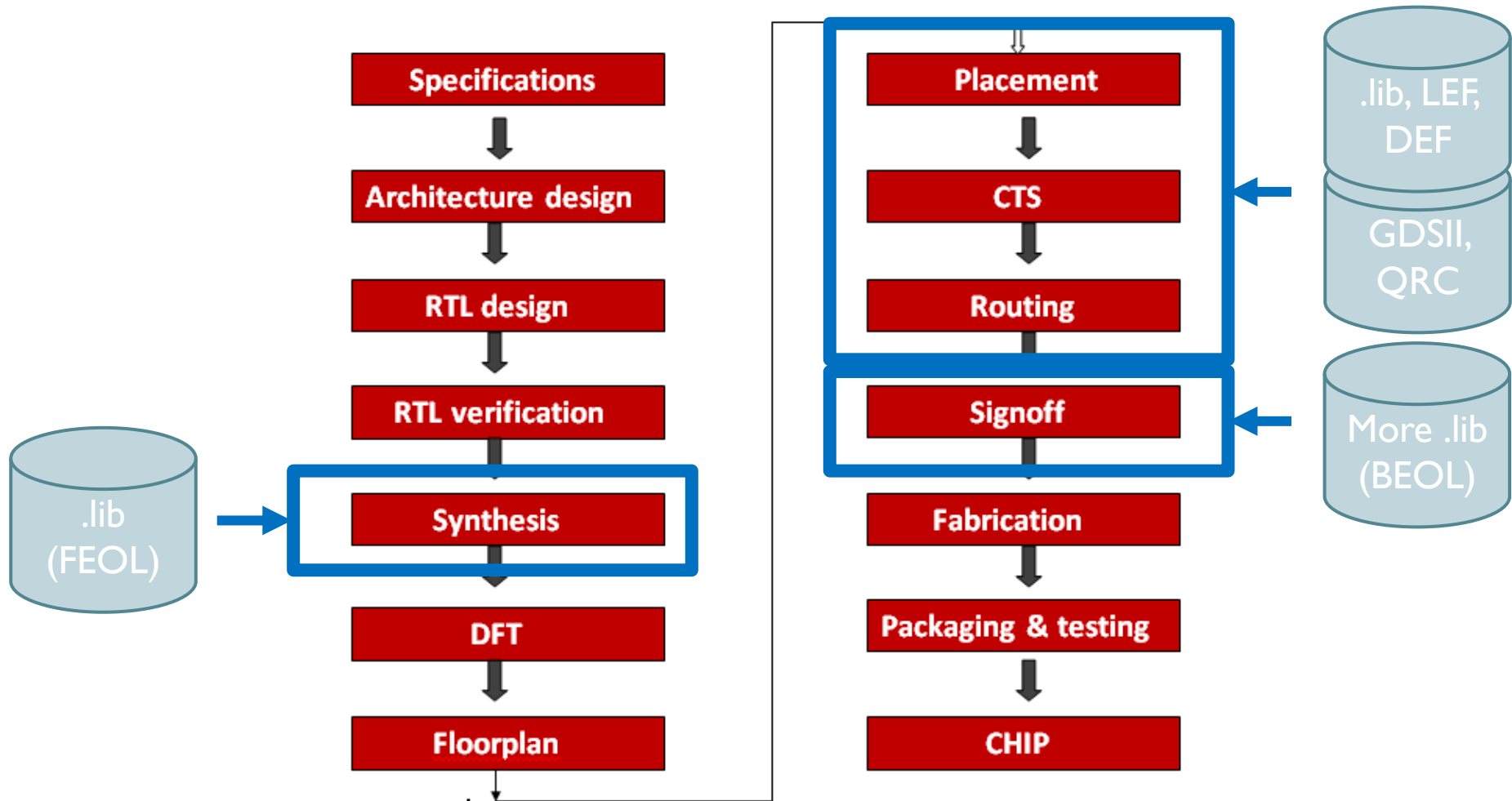

Digital VLSI Systems Components

▶ Combinational Elements:

 - ▶ Implement stateless Boolean functions
 - ▶ Output is always produced upon any input change






Digital VLSI Systems Components

▶ Combinational Elements:

- ▶ Implement stateless Boolean functions

   - ▶ Output is always produced upon any input change




Digital VLSI Systems Components

▶ Sequential Elements:

▶ Implement state

 - ▶ Input is stored
- ▶ Output is produced upon specific triggering events, i.e. clock edges




Digital VLSI Systems Components

▶ Sequential Elements:

▶ Implement state

▶ Input is stored

 ▶ Output is produced upon specific triggering events, i.e. clock edges




Digital VLSI Systems Components

▶ Sequential Elements:

- ▶ Implement state
 - ▶ Input is stored
 - ▶ Output is produced upon spe

Let's count transistors:

 


Digital VLSI Systems Components

▶ Sequential Elements:

▶ Implement state

 - ▶ Input is stored
- ▶ Output is produced upon spe




Digital VLSI Systems Components

▶ Sequential Elements

▶ Implement state

▶ Input is stored

▶ Output is p

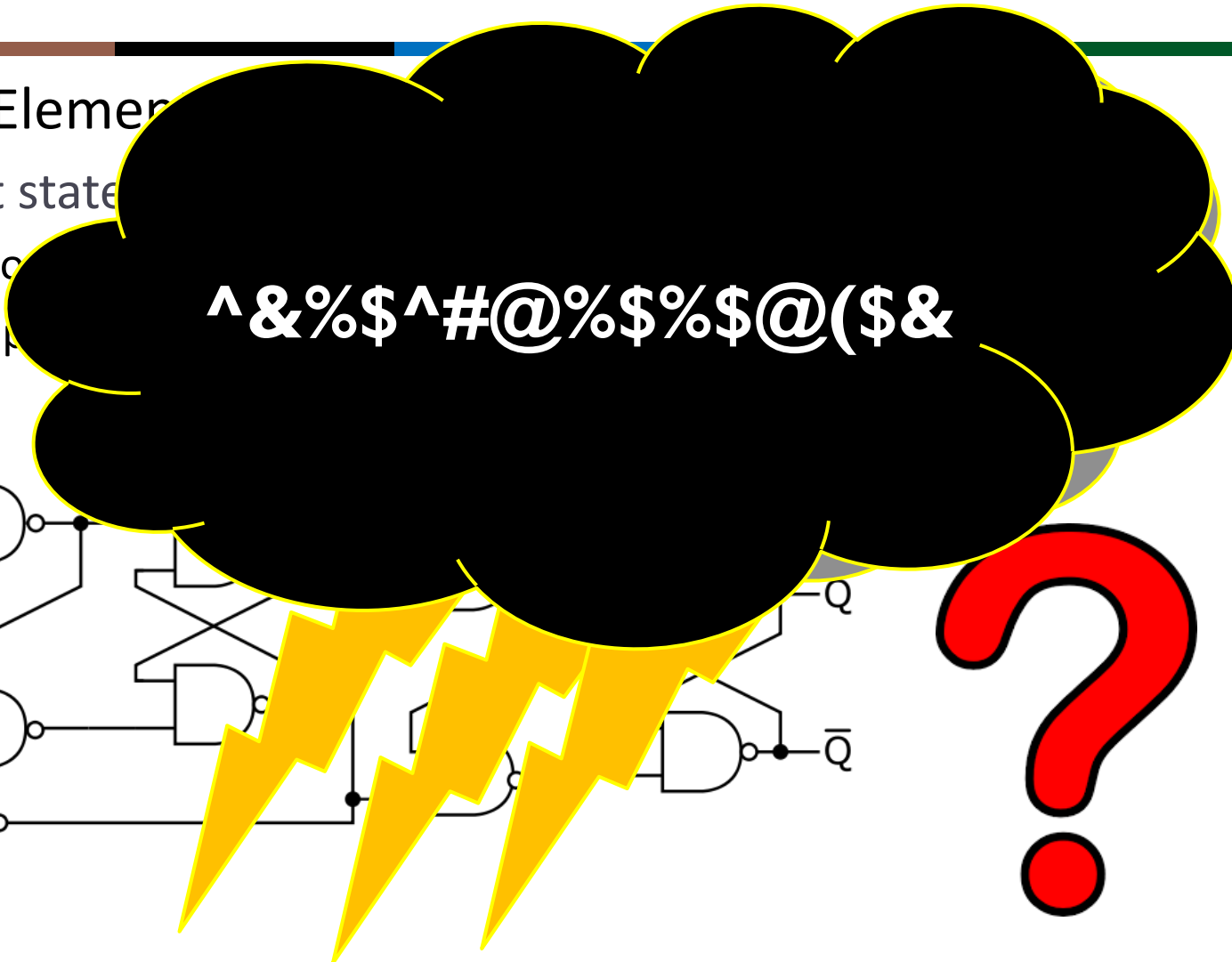


Digital VLSI Systems Components

▶ Sequential Elements:

▶ Implement state

▶ Input is stored

 ▶ Output is produced upon specific triggering events, i.e. clock edges




Digital VLSI Systems Components

▶ Sequential Elements:

- ▶ Implement state
 - ▶ Input is stored
 - ▶ Output is produced upon spe

Let's count transistors:

 


Digital VLSI Systems Components

▶ Sequential Elements:

- ▶ Implement state
 - ▶ Input is stored
 - ▶ Output is produced upon spe

Let's count transistors:

12

 


Digital VLSI Systems Components

▶ Sequential Elements:

- ▶ Implement state
 - ▶ Input is stored
 - ▶ Output is produced upon spe

Let's count transistors:


12

 

Digital VLSI Systems Components


▶ Complex:

- ▶ Implement both state and Boolean operations
 - ▶ Clock Gates

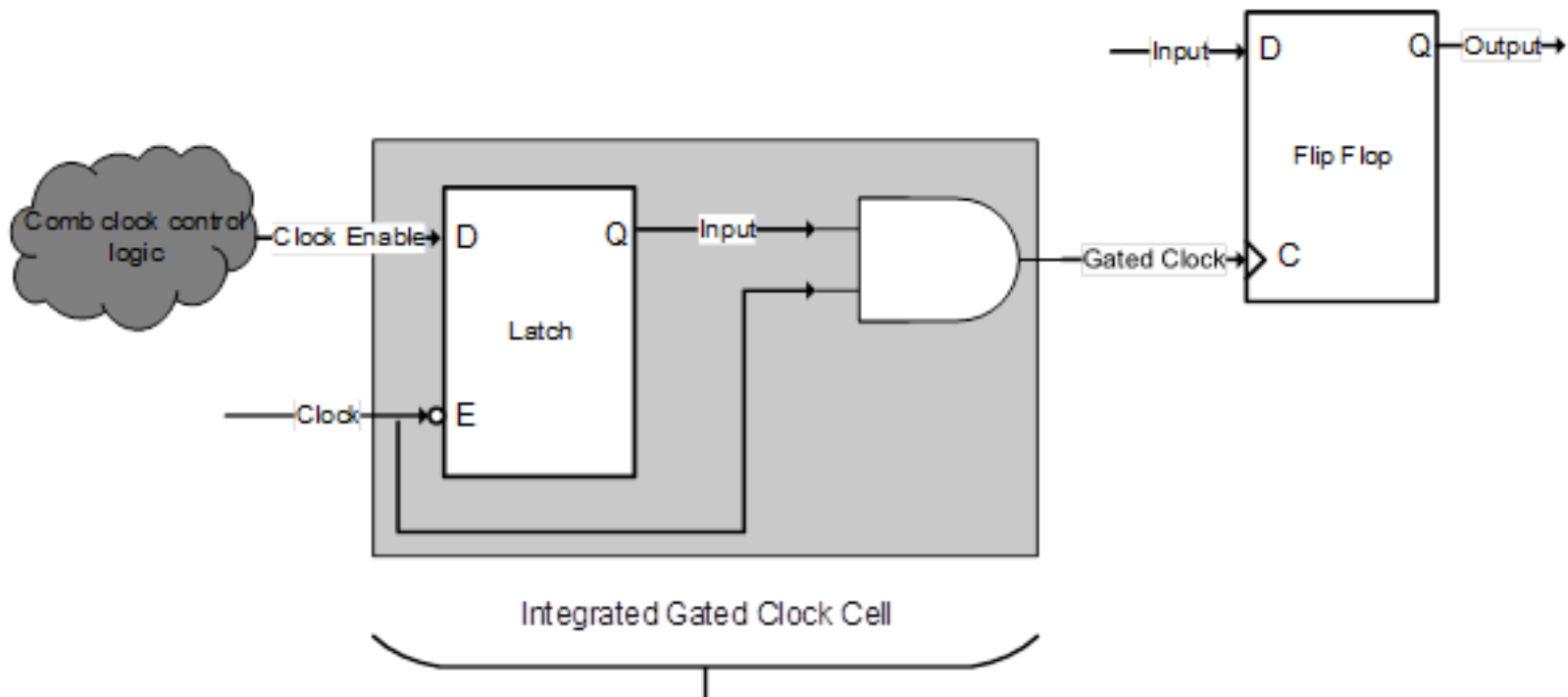

Part I

- ▶ Design DFF, DFFRS standard cells
 - ▶ Create stick diagram
 - ▶ Create layout
 - ▶ Magic or
 - ▶ Microwind or
 - ▶ Cadence IC (Virtuoso) Design Suite or
 - ▶ Synopsys Custom Compiler

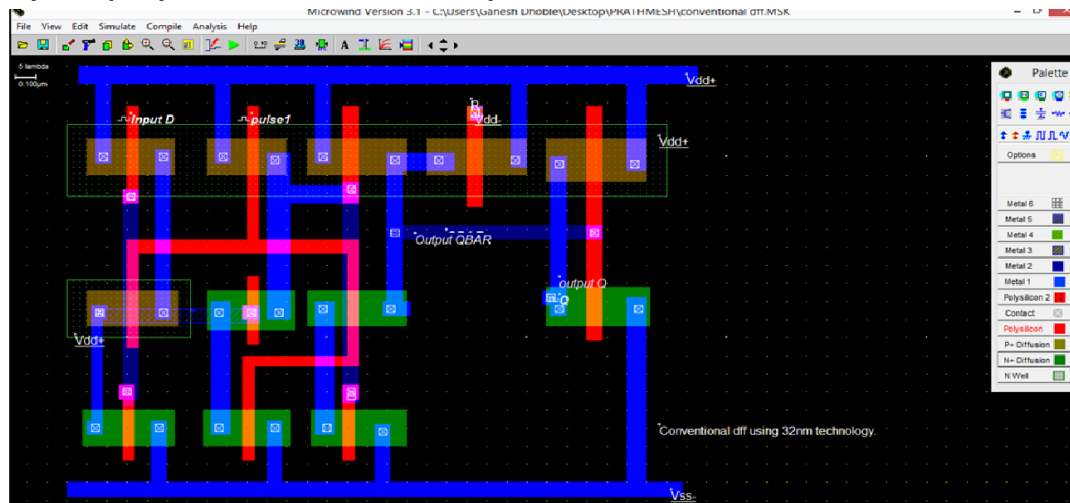

Part I


- ▶ Design XOR/XNOR standard cells
 - ▶ Create stick diagram
 - ▶ Create layout
 - ▶ Magic or
 - ▶ Microwind or
 - ▶ Cadence IC (Virtuoso) Design Suite or
 - ▶ Synopsys Custom Compiler

Part I

- ▶ Layout Extraction
 - ▶ Create SPICE netlist
- ▶ Verify functionality of all aforementioned standard cells
 - ▶ SPICE simulation
 - ▶ How?


Bonus I

 - ▶ Design, extract and verify X1, X4 and X12 cells
 - ▶ What is “drive”?
 - ▶ Differences?



Timing Paths

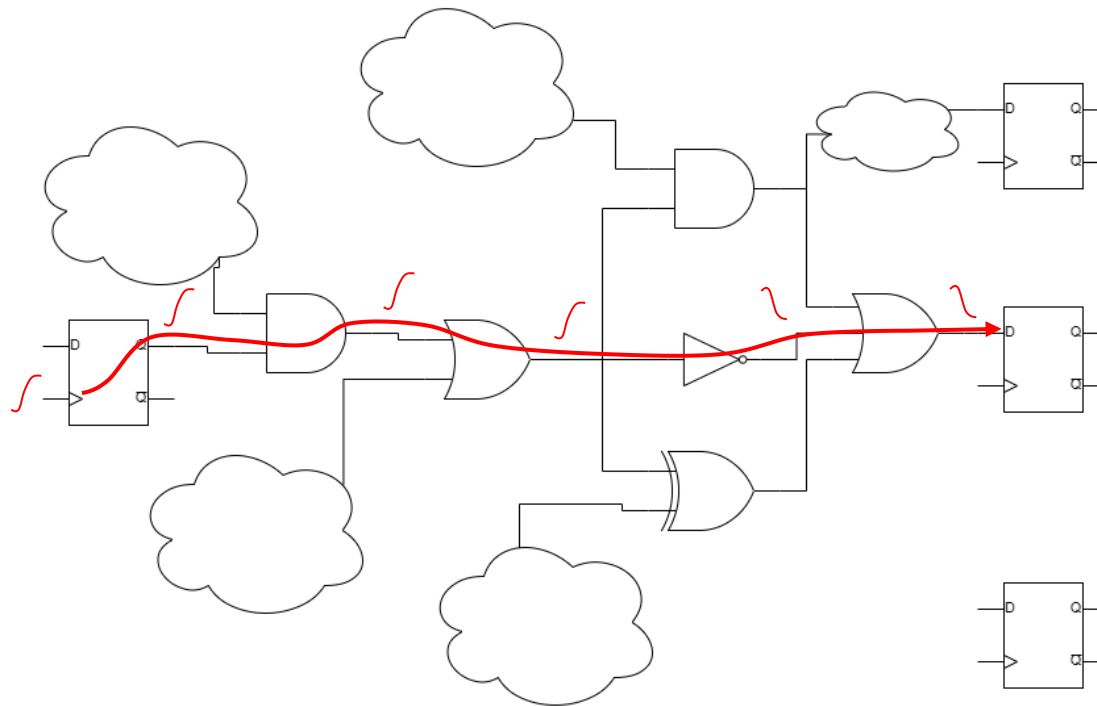
- ▶ Timing paths determine the Performance of our design
 - ▶ Clock frequency



Timing Paths


▶ Four types

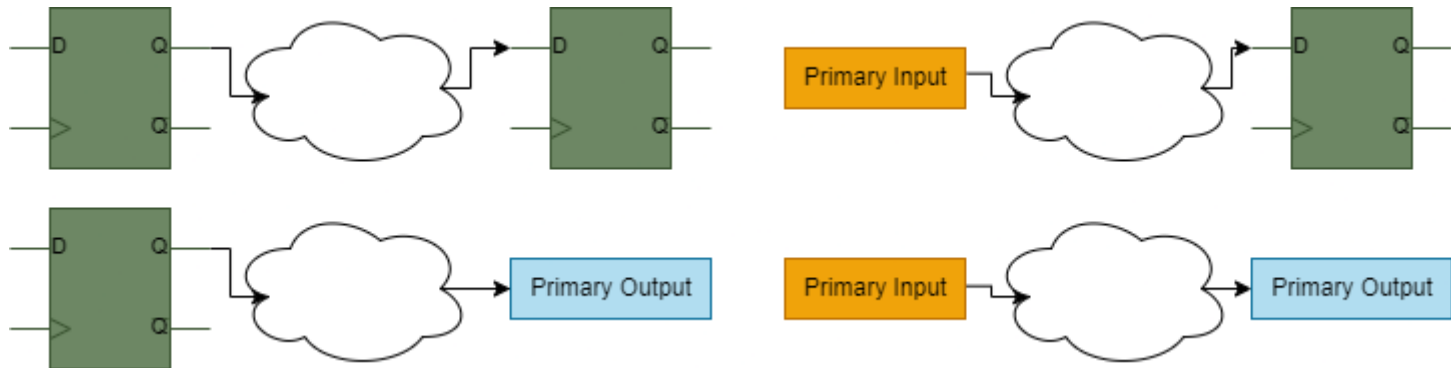- ▶ From Sequential Element to Sequential Element
- ▶ From Sequential Element to Primary Output
- ▶ From Primary Output to Sequential Element
- ▶ From Primary Input to Primary Output



Timing Arcs

 - ▶ Describe timing information from component's input to component's output
 - ▶ Slew
 - ▶ Delay
 - ▶ Unateness





Timing Arcs


▶ Slew

▶ Delay


▶ Unateness

  

Positive Unate

 

Negative Unate

 



Binate

Timing Arcs


▶ Slew

▶ Delay


▶ Unateness

  

Positive Unate

 

Negative Unate

 



Binate

Timing Arcs


▶ Slew

▶ Delay


▶ Unateness

 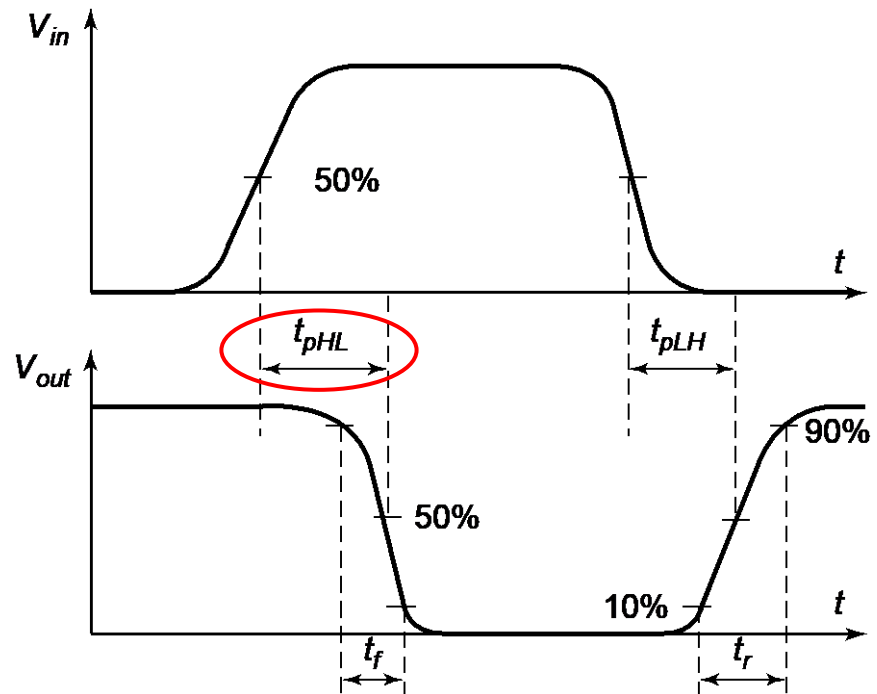

Positive Unate

 

Negative Unate

 



Binate

Timing Arcs

▶ Slew

▶ Delay


▶ Unateness

 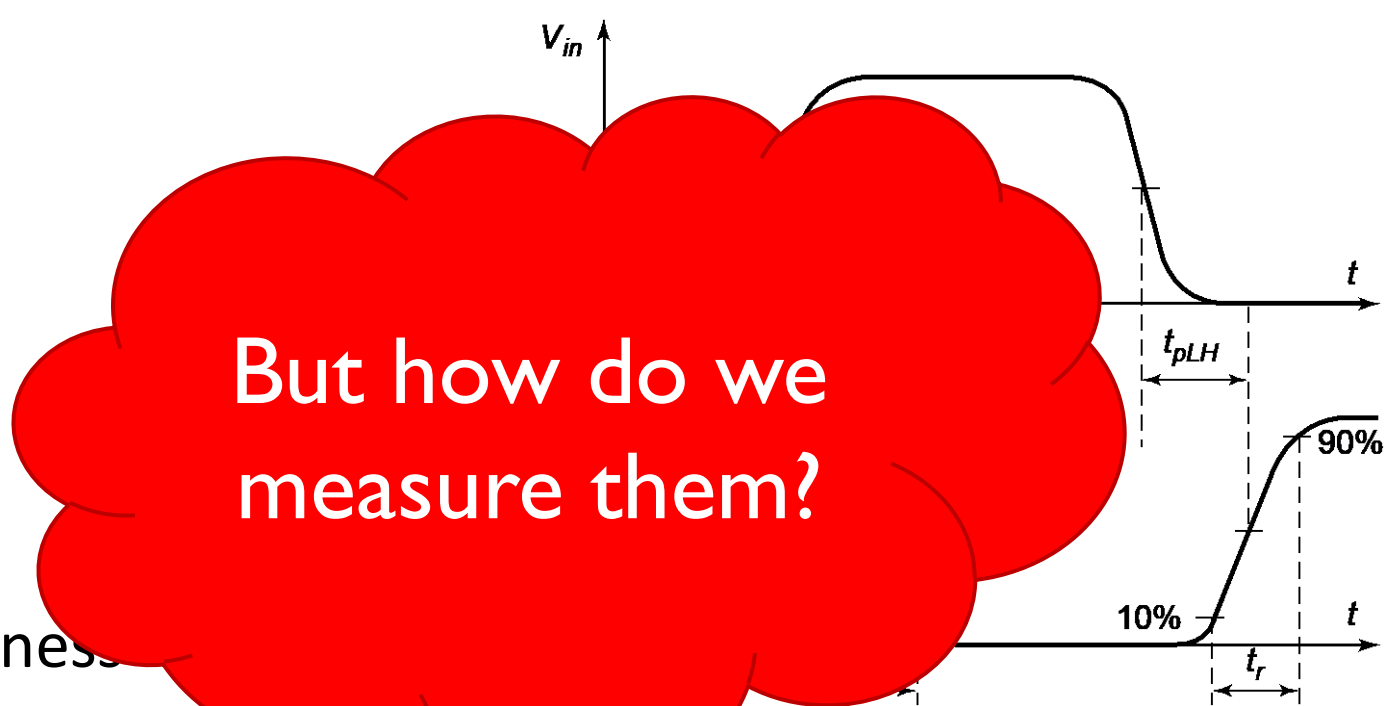

Positive Unate



Negative Unate

 

Binate

SPICE

- ▶ SPICE simulates the design at the device level and measures the required timing information
- ▶ Multiple SPICE tools exist
 - ▶ ng-spice
 - ▶ Synopsys HSPICE
 - ▶ Cadence Spectre

SPICE vs STA

Spice

▶ Pros

- ▶ Accuracy
- ▶ Models all electrical phenomena

▶ Cons

- ▶ Time consuming
 - ▶ Nowadays digital designs consist of million gates
- ▶ Requires input vectors

Static Timing Analysis

▶ Pros

- ▶ Orders of magnitude faster than SPICE
- ▶ Vectorless

▶ Cons

- ▶ Inflicts Pessimism
- ▶ Circuits are DAG
 - ▶ Incompatible with most analog circuits

From SPICE to STA

- ▶ We use SPICE to **characterize** standard cells
 - ▶ Build standard cells layout
 - ▶ Perform SPICE Simulation for multiple vectors (cases)
 - ▶ Store measurement data in file
 - ▶ Liberty File (.lib)
 - ▶ A library of standard cells is created
- ▶ Then STA is applicable on any design consisted of these standard cells
 - ▶ Use .lib file to estimate all cells timing information
 - ▶ Perform all timing checks
 - ▶ Worst case analysis (setup, recovery)
 - ▶ Best case analysis (hold, removal)
 - ▶ Dual mode analysis
 - ▶ Multi-Mode Multi-Corner (MMMC)
 - ▶ Verify no timing violations occur

Liberty File Example

```
27 * Spice engine      : Nanspice v2011.01-HR04-2011-01-19-1102050200
28 * Liberty export type : conditional
29 *
30 * Characterization Corner : worst low
31 * Process              : SlowSlow
32 * Temperature          : -40C
33 * Voltage              : 0.95V
34 *
35 *****/
36
37 library (NangateOpenCellLibrary) {
38
39     /* Documentation Attributes */
40     date          : "Thu 10 Feb 2011, 18:11:08";
41     revision      : "revision 1.0";
42     comment       : "Copyright (c) 2004-2011 Nangate Inc. All Rights Reserved.";
43
44     /* General Attributes */
45     technology    (cmos);
46     delay_model   : table_lookup;
47     in_place_swap_mode : match_footprint;
48     library_features (report_delay_calculation,report_power_calculation);
49
50     /* Units Attributes */
51     time_unit     : "1ns";
52     leakage_power_unit : "1nW";
53     voltage_unit  : "1V";
54     current_unit  : "1mA";
55     pulling_resistance_unit : "1kohm";
56     capacitive_load_unit (1,ff);
57
58     /* Operation Conditions */
59     nom_process   : 1.00;
60     nom_temperature : -40.00;
61     nom_voltage   : 0.95;
62
63     voltage_map (VDD,0.95);
64     voltage_map (VSS,0.00);
65 }
```


Liberty File Example

```
66 define(process_corner, operating_conditions, string);
67 operating_conditions (worst_low) {
68     process_corner : "SlowSlow";
69     process        : 1.00;
70     voltage        : 0.95;
71     temperature    : -40.00;
72     tree_type      : balanced_tree;
73 }
74 default_operating_conditions : worst_low;
75
76 /* Threshold Definitions */
77 slew_lower_threshold_pct_fall : 30.00 ;
78 slew_lower_threshold_pct_rise : 30.00 ;
79 slew_upper_threshold_pct_fall : 70.00 ;
80 slew_upper_threshold_pct_rise : 70.00 ;
81 slew_derate_from_library      : 1.00 ;
82 input_threshold_pct_fall      : 50.00 ;
83 input_threshold_pct_rise      : 50.00 ;
84 output_threshold_pct_fall     : 50.00 ;
85 output_threshold_pct_rise     : 50.00 ;
86 default_leakage_power_density : 0.00 ;
87 default_cell_leakage_power    : 0.00 ;
88
89 /* Default Pin Attributes */
90 default_inout_pin_cap         : 1.000000;
91 default_input_pin_cap         : 1.000000;
92 default_output_pin_cap        : 0.000000;
93 default_fanout_load           : 1.000000;
94 default_max_transition        : 0.179199;
95
96 define(drive_strength, cell, float);
97
98 /* Wire load tables */
99
100 wire_load("1K_hvratio_1_4") {
101     capacitance : 1.774000e-01;
102     resistance  : 3.571429e-03;
```

Liberty File Example

▶ Standard Cell

Library{

...
Cell{

...
Pin {

...
Timing Arc{

...
}
}
}

```
306 cell (AND2_X1) {
307
308     drive_strength      : 1;
309
310     area                : 1.064000;
311     pg_pin(VDD) {
312         voltage_name : VDD;
313         pg_type      : primary_power;
314     }
315     pg_pin(VSS) {
316         voltage_name : VSS;
317         pg_type      : primary_ground;
318     }
319
320
321     cell_leakage_power : 5.607332;
322
323     leakage_power () {
324         when      : "!A1 & !A2";
325         value     : 4.987623;
326     }
327     leakage_power () {
328         when      : "!A1 & A2";
329         value     : 7.256641;
330     }
331     leakage_power () {
332         when      : "A1 & !A2";
333         value     : 4.689846;
334     }
335     leakage_power () {
336         when      : "A1 & A2";
337         value     : 5.495218;
338     }
339
340     pin (A1) {
341
342         direction      : input;
343         related_power_pin : "VDD";
344         related_ground_pin : "VSS";
345         capacitance     : 0.863124;
346         fall_capacitance : 0.825939;
347         rise_capacitance : 0.863124;
348     }
349 }
```

Liberty File Example

▶ Standard Cell

▶ Output Pin

Library{

...

Cell{

...

Pin {

...

Timing Arc{

...

}

}

}

}

```
360 pin (ZN) {
361
362     direction      : output;
363     related_power_pin : "VDD";
364     related_ground_pin : "VSS";
365     max_capacitance  : 60.577400;
366     function        : "(A1 & A2)";
367
368     timing () {
369
370         related_pin      : "A1";
371         timing_sense     : positive_unate;
372
373         cell_fall(Timing_7_7) { ...
374     }
375         cell_rise(Timing_7_7) { ...
376     }
377         fall_transition(Timing_7_7) { ...
378     }
379         rise_transition(Timing_7_7) { ...
380     }
381     }
382
383     timing () {
384
385         related_pin      : "A2";
386         timing_sense     : positive_unate;
387
388         cell_fall(Timing_7_7) { ...
389     }
390         cell_rise(Timing_7_7) { ...
391     }
392         fall_transition(Timing_7_7) { ...
393     }
394         rise_transition(Timing_7_7) { ...
395     }
396     }
397
398     internal_power () {
399
400         related_pin      : "A1";
401         fall_power(Power_7_7) { ...
402     }
403         rise_power(Power_7_7) { ...
404     }
405     }
```

Liberty File Example

- ▶ Standard Cell
 - ▶ Output Pin

Library{

...

Cell{

...

Pin {

...

Timing Arc{

...

}

}

}

}

```
360 pin (ZN) {
361
362     direction : output;
363     related_power_pin : "VDD";
364     related_ground_pin : "VSS";
365     max_capacitance : 60.577400;
366     function : "(A1 & A2)";
367
368     timing () {
369
370         related_pin : "A1";
371         timing_sense : positive_unate;
372
373         cell_fall(Timing_7_7) {
374             index_1 ("0.00123599,0.00443724,0.0156743,0.0371331,0.0705649,0.117474,0.179199");
375             index_2 ("0.365616,1.893040,3.786090,7.572170,15.144300,30.288700,60.577400");
376             values ("0.0197041,0.0229342,0.0261342,0.0316819,0.0418923,0.0618128,0.101536", \
377                 "0.0216364,0.0248607,0.0280608,0.0336097,0.0438212,0.0637433,0.103464", \
378                 "0.0289835,0.0321848,0.0353744,0.0409242,0.0511493,0.0710896,0.110815", \
379                 "0.0425898,0.0460109,0.0492983,0.0548991,0.0651351,0.0850696,0.124801", \
380                 "0.0580821,0.0621944,0.0659897,0.0720759,0.0825757,0.102509,0.142163", \
381                 "0.0742902,0.0791617,0.0835824,0.0904105,0.101391,0.121440,0.161074", \
382                 "0.0910191,0.0966479,0.101747,0.109470,0.121270,0.141603,0.181147");
383         }
384         cell_rise(Timing_7_7) {
385             index_1 ("0.00123599,0.00443724,0.0156743,0.0371331,0.0705649,0.117474,0.179199");
386             index_2 ("0.365616,1.893040,3.786090,7.572170,15.144300,30.288700,60.577400");
387             values ("0.0230298,0.0270509,0.0312284,0.0388180,0.0533003,0.0818721,0.138814", \
388                 "0.0245601,0.0285814,0.0327573,0.0403454,0.0548287,0.0834065,0.140348", \
389                 "0.0304245,0.0344326,0.0385950,0.0461608,0.0606317,0.0892160,0.146174", \
390                 "0.0409252,0.0450782,0.0492911,0.0568521,0.0712874,0.0998537,0.156828", \
391                 "0.0518173,0.0566106,0.0609955,0.0686033,0.0830503,0.111620,0.168548", \
392                 "0.0618256,0.0675495,0.0725313,0.0803659,0.0946294,0.123097,0.180075", \
393                 "0.0705818,0.0772655,0.0830771,0.0915994,0.105779,0.134024,0.190909");
394         }
395         fall_transition(Timing_7_7) {
396             index_1 ("0.00123599,0.00443724,0.0156743,0.0371331,0.0705649,0.117474,0.179199");
397             index_2 ("0.365616,1.893040,3.786090,7.572170,15.144300,30.288700,60.577400");
398             values ("0.00351368,0.00506123,0.00691963,0.0107244,0.0187465,0.0354498,0.0691994", \
399                 "0.00351248,0.00506106,0.00692003,0.0107248,0.0187469,0.0354503,0.0691987", \
400                 "0.00352519,0.00507910,0.00693509,0.0107318,0.0187484,0.0354500,0.0691960", \
401                 "0.00423906,0.00560331,0.00727993,0.0108921,0.0187916,0.0354532,0.0691983", \
402                 "0.00583849,0.00719476,0.00874388,0.0119833,0.0193276,0.0355537,0.0691968", \
403                 "0.00769208,0.00913953,0.0106799,0.0136464,0.0203254,0.0359792,0.0693179", \
404                 "0.00973624,0.0113139,0.0129445,0.0158442,0.0218882,0.0365848,0.0695901");
```

Liberty File Example

- ▶ Standard Cell
 - ▶ Sequential cell
 - ▶ Constraint Arcs


```
Library{  
  ...  
  Cell{  
    ...  
    Pin {  
      ...  
      Timing Arc{  
        ...  
      }  
    }  
  }  
}
```

```
cell (DFFRS_X1) {  
  drive_strength      : 1;  
  
  ff ("IQ" , "IQN") {  
    next_state       : "D";  
    clocked_on       : "CK";  
    preset           : "!SN";  
    clear            : "!RN";  
    clear_preset_var1 : L;  
    clear_preset_var2 : L;  
  }  
  
  pin (D) {   
  }  
  
  pin (RN) {   
  }  
  
  pin (SN) {   
  }  
  
  pin (CK) {   
  }  
  
  pin (Q) {   
  }  
  
  pin (QN) {   
  }  
  
}
```

```
cell (DFFRS_X1) {  
  drive_strength      : 1;  
  
  ff ("IQ" , "IQN") {  
    next_state       : "D";  
    clocked_on       : "CK";  
    preset           : "!SN";  
    clear            : "!RN";  
    clear_preset_var1 : L;  
    clear_preset_var2 : L;  
  }  
  
  pin (D) {  
    direction        : input;  
    related_power_pin : "VDD";  
    related_ground_pin : "VSS";  
    capacitance       : 1.090003;  
    fall_capacitance  : 1.024518;  
    rise_capacitance  : 1.090003;  
  
    timing () {  
      related_pin      : "CK";  
      timing_type      : hold_rising;  
      when              : "RN & SN";  
      sdf_cond         : "RN AND SN === 1'b1";  
      fall_constraint(Hold_3_3) {   
      }  
      rise_constraint(Hold_3_3) {   
      }  
    }  
  
    timing () {  
      related_pin      : "CK";  
      timing_type      : setup_rising;  
      when              : "RN & SN";  
      sdf_cond         : "RN AND SN === 1'b1";  
      fall_constraint(Setup_3_3) {   
      }  
      rise_constraint(Setup_3_3) {   
      }  
    }  
  
    internal_power () {  
    }  
  }  
}
```

Timing Calculations

 - ▶ Output slew and delay calculation using .lib data
- ▶ Calculation is performed based on
 - ▶ Input slew
 - ▶ Output load




NLDM Driver Model

		cell_fall	fall_transition								
S_{drv}^{in}	C_{drv}^{out}	<table border="1"><tr><td>0.1</td><td>0.2</td></tr><tr><td>0.4</td><td>0.5</td></tr></table>	0.1	0.2	0.4	0.5	<table border="1"><tr><td>0.1</td><td>0.2</td></tr><tr><td>0.4</td><td>0.5</td></tr></table>	0.1	0.2	0.4	0.5
	0.1	0.2									
0.4	0.5										
0.1	0.2										
0.4	0.5										

Timing Calculations

 - ▶ Output slew and delay calculation using .lib data
- ▶ Calculation is performed based on
 - ▶ Input slew
 - ▶ Output load




NLDM Driver Model


	cell_fall	fall_transition												
S_{in_drv}	<table border="1"><thead><tr><th>C_{out_drv}</th><th>0.1</th><th>0.2</th></tr></thead><tbody><tr><th>0.4</th><td>0.4</td><td>0.5</td></tr></tbody></table>	C_{out_drv}	0.1	0.2	0.4	0.4	0.5	<table border="1"><thead><tr><th>C_{out_drv}</th><th>0.1</th><th>0.2</th></tr></thead><tbody><tr><th>0.4</th><td>0.4</td><td>0.5</td></tr></tbody></table>	C_{out_drv}	0.1	0.2	0.4	0.4	0.5
C_{out_drv}	0.1	0.2												
0.4	0.4	0.5												
C_{out_drv}	0.1	0.2												
0.4	0.4	0.5												

Timing Calculations

 - ▶ Output slew and delay calculation using .lib data
- ▶ Calculation is performed based on
 - ▶ Input slew
 - ▶ Output load




NLDM Driver Model

 

Timing Calculations

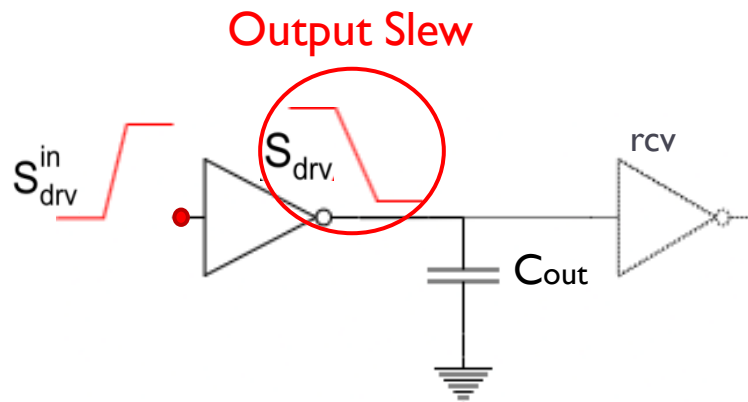- ▶ Output slew and delay calculation using .lib data
- ▶ Calculation is performed based on
 - ▶ Input slew
 - ▶ Output load



NLDM Driver Model



	cell_fall	fall_transition																		
S_{drv}^{in}	<table border="1"><thead><tr><th>C_{drv}^{out}</th><th>0.1</th><th>0.2</th></tr></thead><tbody><tr><th>0.4</th><td>0.1</td><td>0.2</td></tr><tr><th>0.5</th><td>0.4</td><td>0.5</td></tr></tbody></table>	C_{drv}^{out}	0.1	0.2	0.4	0.1	0.2	0.5	0.4	0.5	<table border="1"><thead><tr><th>C_{drv}^{out}</th><th>0.1</th><th>0.2</th></tr></thead><tbody><tr><th>0.4</th><td>0.1</td><td>0.2</td></tr><tr><th>0.5</th><td>0.4</td><td>0.5</td></tr></tbody></table>	C_{drv}^{out}	0.1	0.2	0.4	0.1	0.2	0.5	0.4	0.5
C_{drv}^{out}	0.1	0.2																		
0.4	0.1	0.2																		
0.5	0.4	0.5																		
C_{drv}^{out}	0.1	0.2																		
0.4	0.1	0.2																		
0.5	0.4	0.5																		



Timing Checks


- ▶ Timing constraints are imposed to Sequential std. cells
 - ▶ To ensure correct functionality
- ▶ Such constraints are Setup, Hold, Recovery and Removal time
 - ▶ STA tools perform timing checks to ensure no violations will happen

Data Launch and Capture

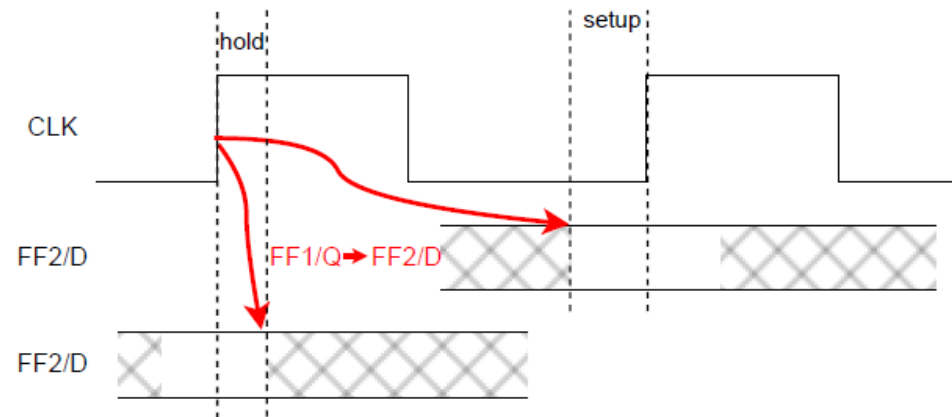 


Data Launch and Capture

- ▶ For Setup Timing Check:

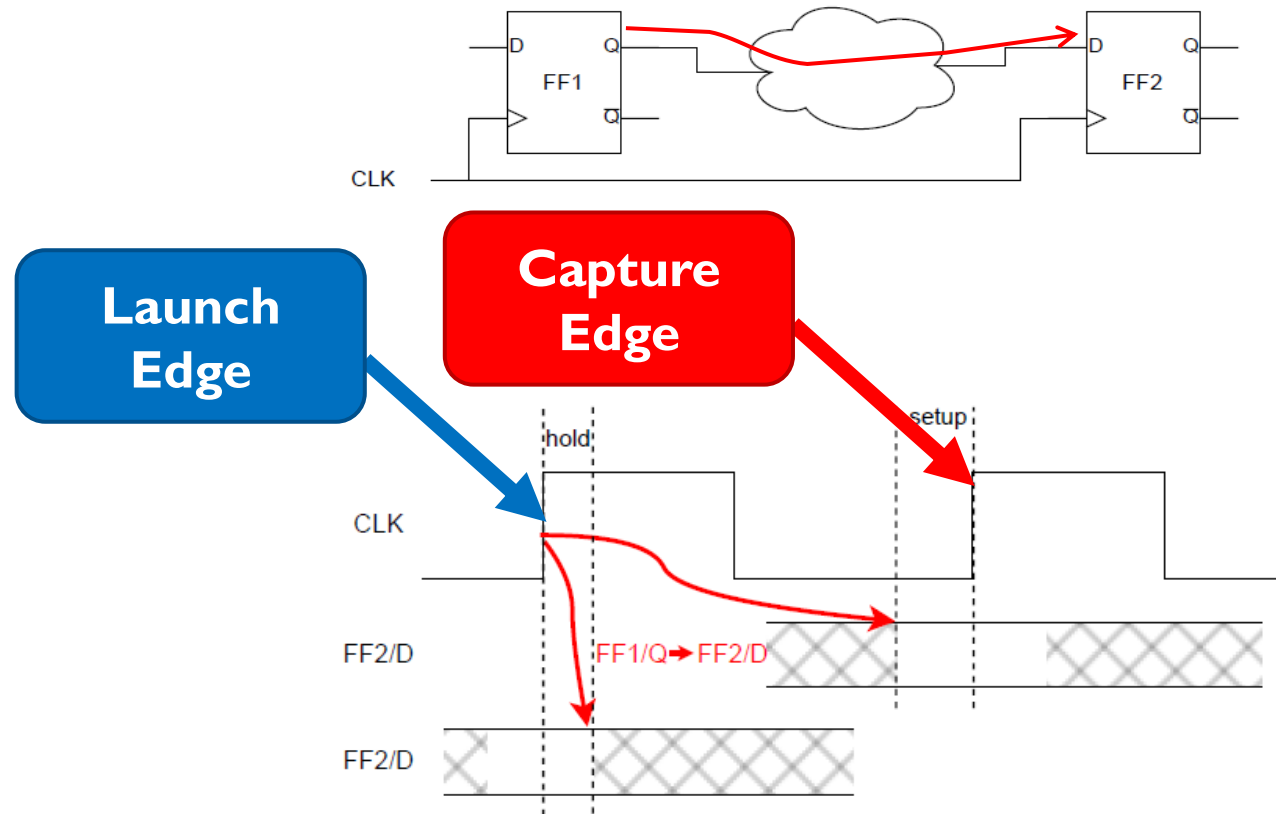

Data Launch and Capture


► For Hold Timing Check:

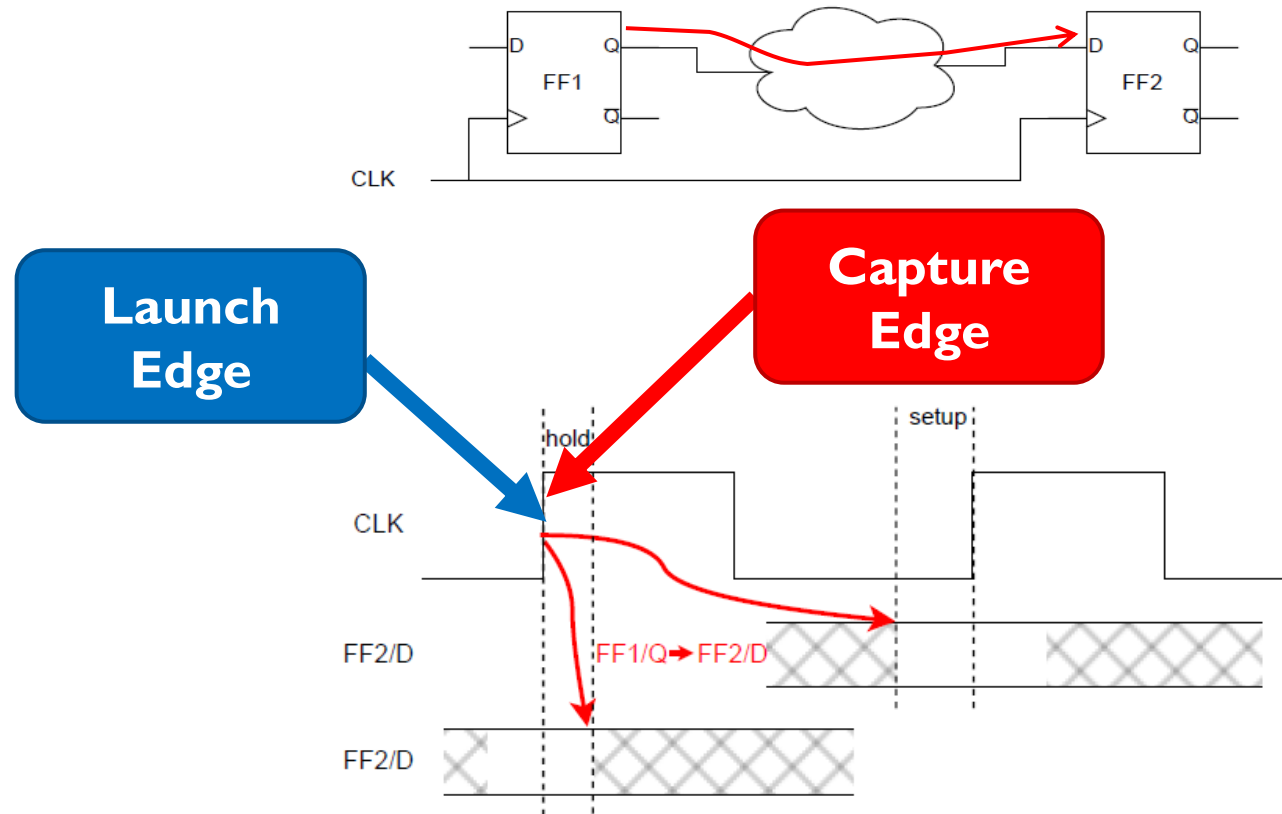

Timing Checks


▶ Setup timing check

 - ▶ Data must arrive to path endpoint, before a specific time margin from next clock active edge



▶ Hold timing check

 - ▶ Data must remain stable at path endpoint, for a specific time margin after the same clock active edge, which triggered data launch




Timing Checks

▶ Recovery timing check

- ▶ Reset should arrive before a specific time margin from next active clock edge
- ▶ Resembles Setup timing check

▶ Removal timing check

- ▶ Reset should arrive after a specific time margin from last active clock edge
- ▶ Resembles Hold timing check

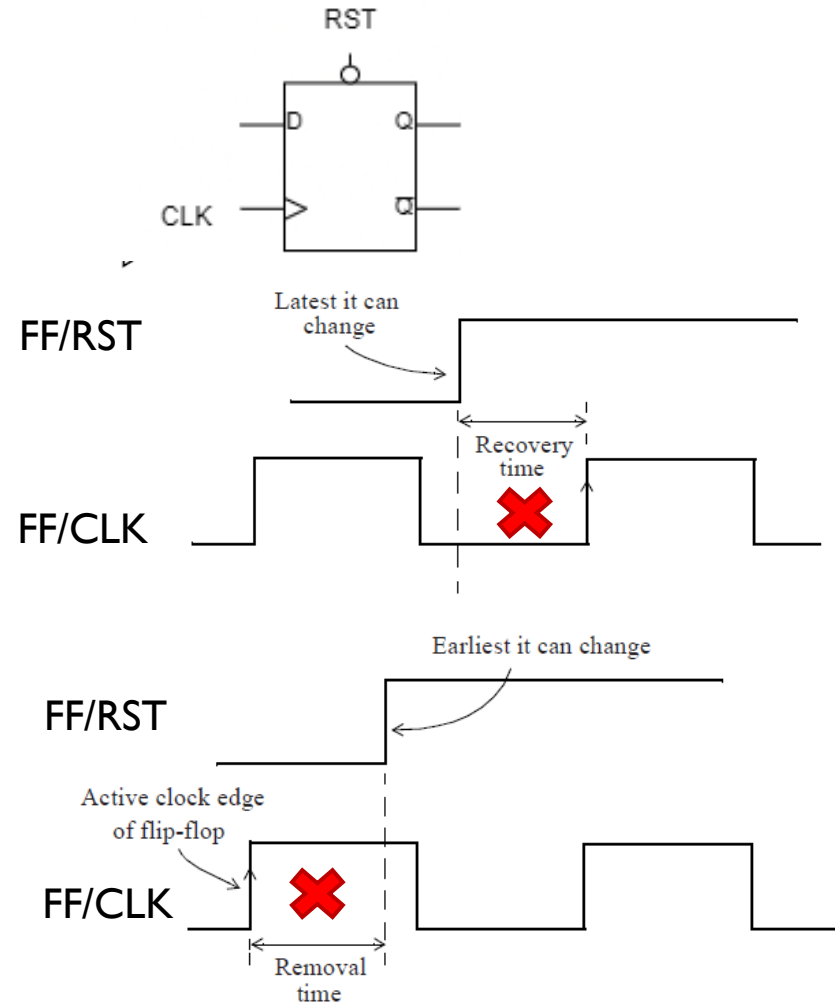

Part II

- ▶ Create C/C++/Python/Bash program
 - ▶ Use extracted SPICE deck (magic, ext2spice) from Part I
 - ▶ Run SPICE for multiple stimulus and load combinations
 - ▶ 1 run per input slew, output load pair
 - ▶ Measure delay and slew
 - ▶ Store measurement data
 - ▶ Tools:
 - ng-spice/Xyce/HSPICE/Spectre
 - ▶ Calculate setup, hold, recovery, removal times for Flip-Flops
 - ▶ Trial and error methodology
 - ▶ Write measurement data to your own custom Liberty File (.lib)
 - ▶ You will be provided with a template Liberty File
 - ▶ You will only need to write specific fields, NOT the entire file from scratch

Verilog



- ▶ Verilog is one of the 2 most widespread Hardware Description Languages (HDLs)

Verilog



- ▶ Verilog is one of the 2 most widespread Hardware Description Languages (HDLs)
 - ▶ The other one being VHDL



Verilog



- ▶ Verilog is one of the 2 most widespread Hardware Description Languages (HDLs)
 - ▶ The other one being VHDL
- ▶ We will only use it in its Gate-Level Netlist form
 - ▶ Wires
 - ▶ Standard cell instantiations
 - ▶ I/O ports and top module declaration

```
module counter_DW01_inc_0 ( A, SUM );
  input [7:0] A;
  output [7:0] SUM;

  wire [7:2] carry;


  HAJIX0 U1_1_6 ( .A(A[6]), .B(carry[6]), .CO(carry[7]), .S(SUM[6]) );
  HAJIX0 U1_1_5 ( .A(A[5]), .B(carry[5]), .CO(carry[6]), .S(SUM[5]) );
  HAJIX0 U1_1_4 ( .A(A[4]), .B(carry[4]), .CO(carry[5]), .S(SUM[4]) );
  HAJIX0 U1_1_3 ( .A(A[3]), .B(carry[3]), .CO(carry[4]), .S(SUM[3]) );
  HAJIX0 U1_1_2 ( .A(A[2]), .B(carry[2]), .CO(carry[3]), .S(SUM[2]) );
  HAJIX0 U1_1_1 ( .A(A[1]), .B(A[0]), .CO(carry[2]), .S(SUM[1]) );
  INVJIX0 U1 ( .A(A[0]), .Q(SUM[0]) );
  E02JIX0 U2 ( .A(carry[7]), .B(A[7]), .Q(SUM[7]) );
endmodule
```

Part III

- ▶ Use the std. cells you created and characterized in Parts I & II and create a Verilog module which contains
 - ▶ 2 8-bit registers
 - ▶ A comparator which compares the above registers
 - ▶ 1 register to store the comparator result

Part III

- ▶ Use the std. cells you created and characterized in Parts I & II and create a Verilog module which contains
 - ▶ 2 8-bit registers
 - ▶ A comparator which compares the above registers
 - ▶ 1 register to store the comparator result

 

Part III

- ▶ Create Verilog `'specify'` blocks for the std. cells you created
- ▶ Create Testbench and make sure your design is functioning properly
 - ▶ Tools: Modelsim
- ▶ Use an STA engine to analyze timing
 - ▶ We will provide you with the script
 - ▶ Tools:
 - ▶ OpenROAD OpenSTA
 - ▶ Synopsys PrimeTime
 - ▶ Cadence Tempus
- ▶ Find the critical path of your design

Bonus II

- ▶ Use the higher drive std. cells you created in Bonus I
 - ▶ Optimize your design for highest possible performance
 - ▶ Try to perform area recovery
- ▶ Comment on your thought process and efforts to achieve the above