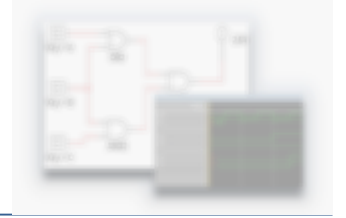


ECE119 – Ψηφιακή Σχεδίαση

Διδάσκοντες Εργαστηρίου: Δ. Καραμπερόπουλος
Δ. Γαρυφάλλου


➤ Lab 9: Flip-Flops

Περιεχόμενα Εργαστηριακού Μαθήματος




- Εισαγωγή
- Lab 1: Multisim Circuit Simulation and Basic Gates
- Lab 2: Truth Tables and Basic Logic Gates
- Lab 3: Logic Gates Explored and Boolean Algebra
- Lab 4: Karnaugh Maps
- Lab 5: Binary Conversion and Adders
- Lab 6: Encoders and Decoders
- Lab 7: Multiplexers and Demultiplexers
- Lab 8: Latches and Sequential Logic Circuits
- **Lab 9: Flip-Flops**
- Lab 10: Sequential Circuits - FSM

Flip-Flops

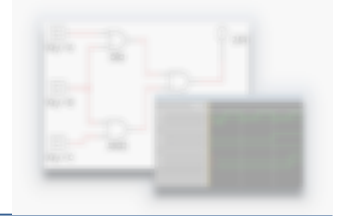

- In the previous lab, you were introduced to the concept of sequential logic circuits by examining **latches**.
- Particularly, you explored **D and SR latches**.
- In this lab, you will explore sequential logic circuits by focusing on **flip-flops**.
- **Flip flops** differ from latches in that they are **edge triggered**.
- **Latches** are **level sensitive** devices.
- Flip-flops can be constructed from latches.
- Together, flip-flops and latches are the building blocks of sequential logic circuits.


Learning Objectives

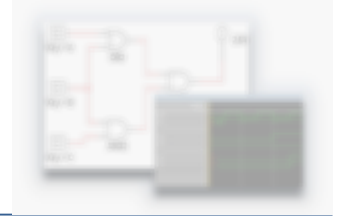

In this lab, students will:

- Become familiar with the basic behavior of **D, JK** and **T flip-flops**
- Explore variations of flip-flops in greater detail (i.e. master-slave relationships)
- Gain an awareness of the versatility of the DFF and its application in other circuits.


Expected Deliverables

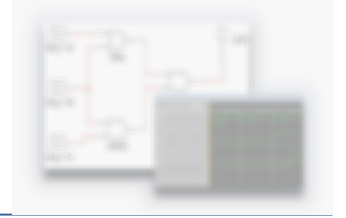

In this lab, you will collect the following deliverables:

- Flip-flop analysis
- Conclusion questions

Flip-Flops

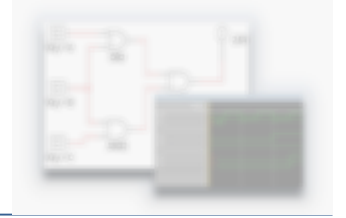

- Flip-flops are the fundamental building blocks of sequential circuits.
- They are **1-bit storage devices** that, unlike latches (which are level sensitive devices) are **edge-triggered**.
- Data gets stored into a flip-flop **at one of the edges** of the clock signal, i.e. when the clock input makes a transition from 0 to 1 or from 1 to 0.



(a) Response to positive level




(b) Positive-edge response




(c) Negative-edge response


Latch Feedback

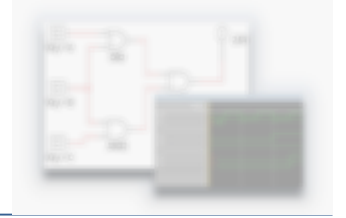

- The state transitions of the latches start in the moment the clock changes to 1 and can continue for the entire period while it is active.
- Because of this, the output of a latch cannot be applied through combinational circuits to the inputs of other latches triggered by the same clock signal.
- This fact represents a **serious drawback** when using latches as storage elements.
- **Flip-flops** overcome this problem by **triggering only during signal changes (edges)**.

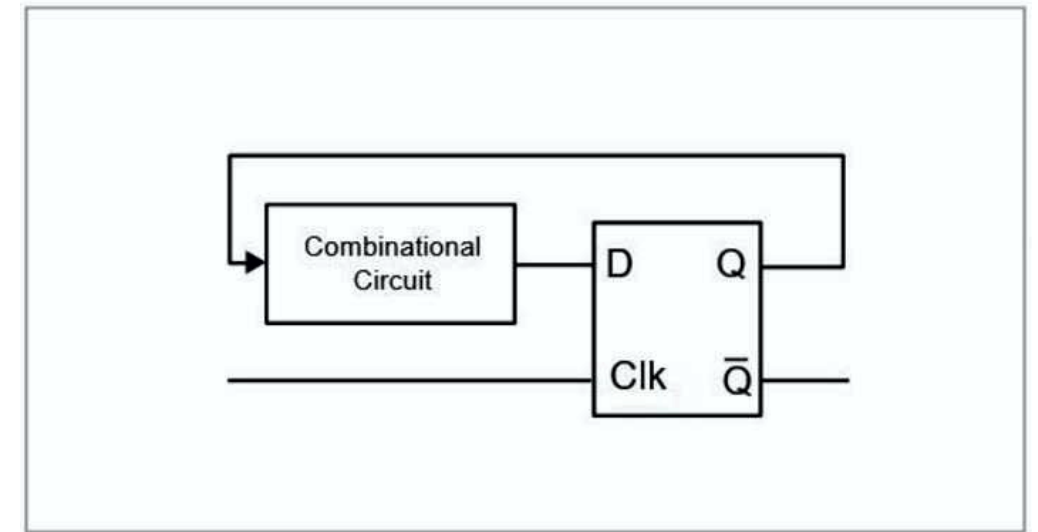


D Flip-flops (DFFs)

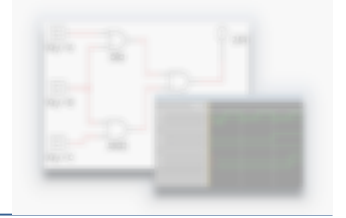


D flip-flops (DFFs) are very commonly used because they are perfectly suited for the construction of sequential circuits.

 - If the DFF transfers the input to the output on the **rising edge** of the clock signal then it is said to be a positive-edge triggered D flip-flop or **positive-edge DFF**.
- If the DFF transfers the input to the output on the **falling edge** of the clock signal then it is said to be a negative-edge triggered D flip-flop or **negative-edge DFF**.




D Flip-flops (DFFs)


- This mode of operation is signaled through the use of a **circle** on the **clock input**. The image below shows the symbol for a positive-edge DFF (left) and a negative-edge DFF (right).
- For both DFF circuits shown below, the **small triangle** on the **clock input** indicates that the flip-flop will trigger only on one of the **clock edges**.
- The complemented output, Q is omitted in the graphical symbol when it is not needed.

 

Positive edge DFF

 

negative edge DFF

 

D Flip-flops (DFFs)


The operation of the **positive-triggered D flip-flop** is very simple:

- The output Q will go to the present state of the D input when the clock signal **changes from 0 to 1**
- The level present at the input will be stored in the flip-flop on the **rising transition** of the Clk signal.
- The figures below present the functionality of a positive-edge DFF:


Χαρακτηριστική εξίσωση

$$Q(t+1) = D$$

Clk	Q(t + 1)
0	Q
1	Q
↑	D
↓	Q

 


D Flip-Flop		
D	Q(t + 1)	
0	0	Reset
1	1	Set

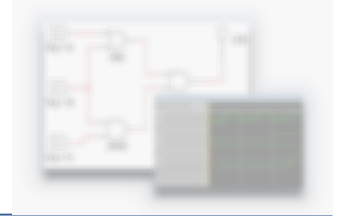

D Flip-flops (DFFs)


A flip-flop can be built using the following methods:

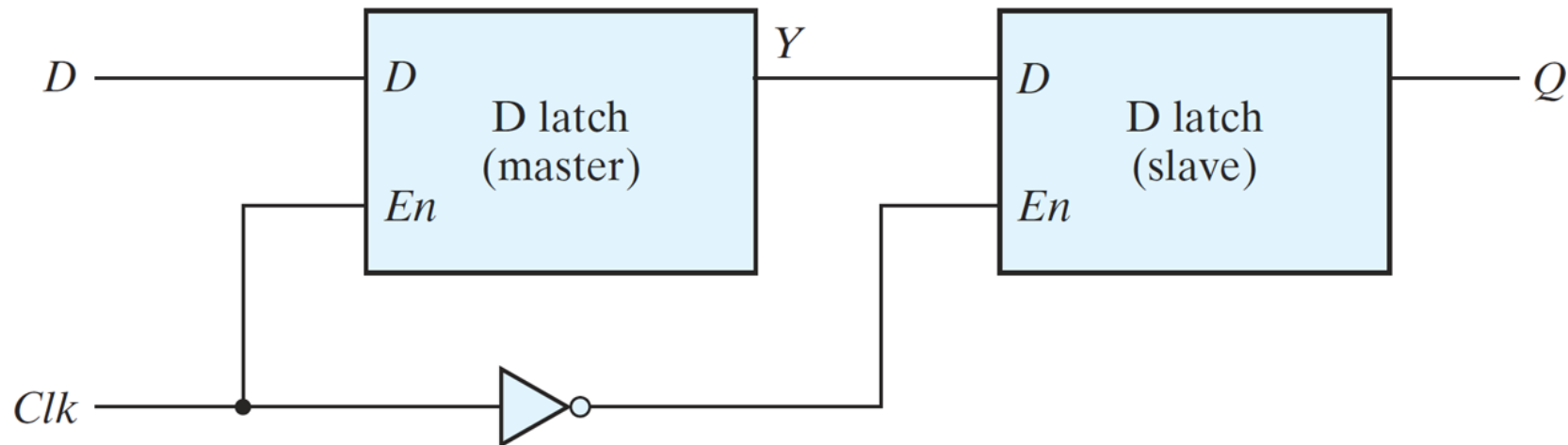- Using **two D latches** arranged in a **master-slave** configuration, where one of them is transparent during one semi-period of the clock period and the other transparent during the other semi-period.




D Flip-flops (DFFs)

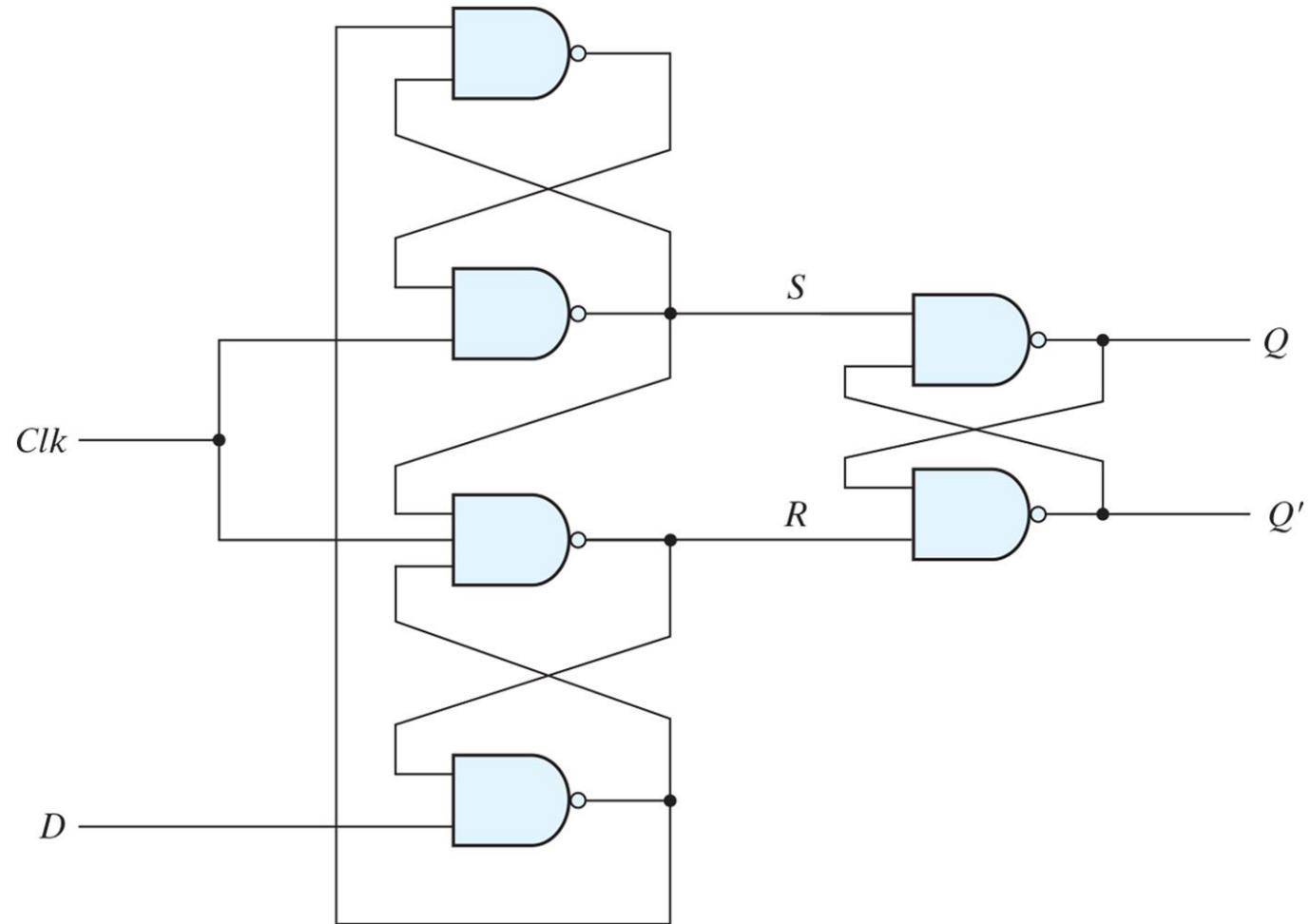- Another circuit having the same operation, but implemented using fewer gates, can be built from **three SR latches**.




Flip-flops

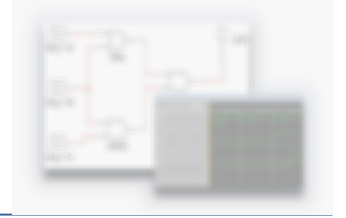

The timing characteristics of flip-flops include:

- the **propagation delay (χρόνος καθυστέρησης διάδοσης)** from Clk to Q (the time needed for a value present on the input to reach the output when the clock changes from 0 to 1)
- the **setup time (χρόνος προετοιμασίας)**
- the **hold time (χρόνος συγκράτησης)**
- the **maximum frequency** that can be applied to the clock signal and still have correct operation


JK Flip-flop (JKFF)

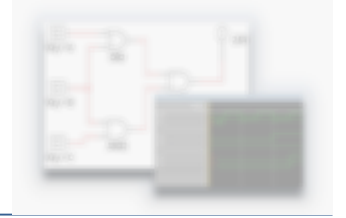

Another type of flip-flop, one that is not as widely used as the DFF, but a more versatile one, is the **J K flip-flop (JKFF)**.

- The J K flip-flop is referred to as the **universal bi-stable** because it can easily behave like any one of the others.
- It has **two data inputs**, (**J and K**), a clock input, and two outputs (Q and \bar{Q})
- **J acts as a SET** input and **K acts as a RESET** input.
- The output changes only on one of the **clock edges**.
- When both **J and K are 1**, the flip-flop **toggles** between opposite logic states each time the clock signal changes from 0 to 1 or from 1 to 0.
- This circuit is like the one of a gated SR latch with an edge detector, with the difference that the forbidden state (when both S and R are set to 1) is replaced by the toggle state.

JK Flip-flop (JKFF)

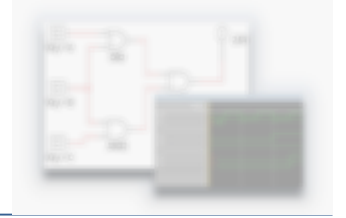

The golden rules of JKFFs are:


- If **J** and **K** are **0**, nothing happens.
- If **J** and **K** are **1**, **Q** toggles.
- If **J** and **K** are **different**, then **Q** is always the same as **J**.

Χαρακτηριστική εξίσωση

$$Q(t+1) = J Q' + K' Q$$


JK Flip-Flop

J	K	Q(t + 1)	
0	0	$Q(t)$	No change
0	1	0	Reset
1	0	1	Set
1	1	$Q'(t)$	Complement

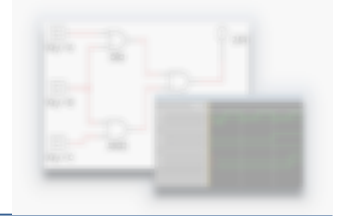


JK Flip-flop (JKFF)

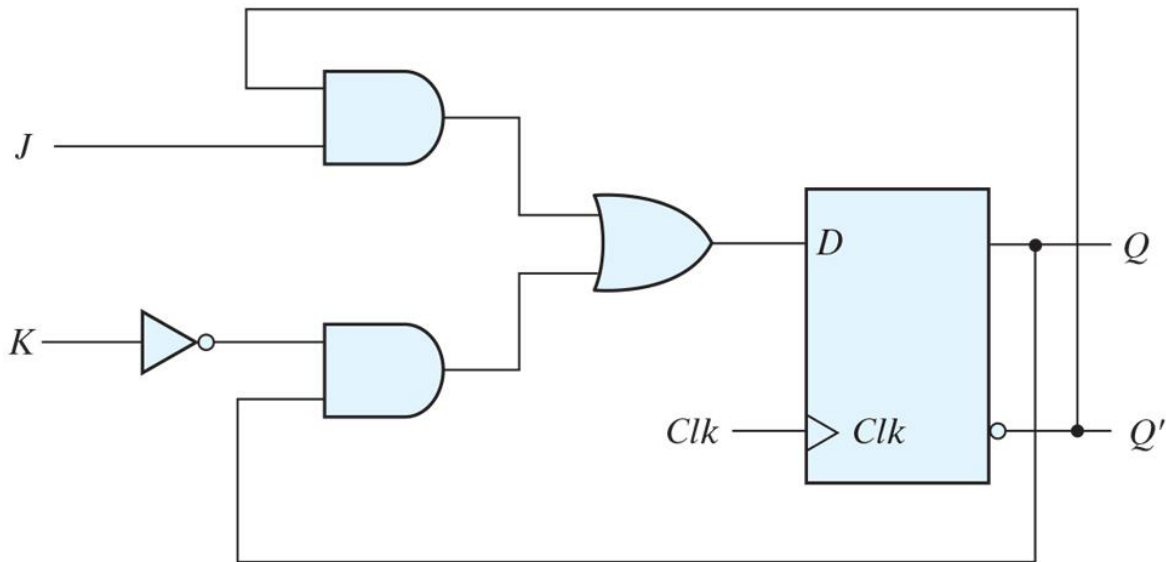- The figures below present the way in which a J K flip-flop can be built using a DFF and logic gates. The graphical symbol of the JKFF is also shown below, and its operation is described by the characteristic table



(a) Circuit diagram


$$D = JQ' + K'Q$$

 

(b) Graphic symbol

JK Flip-Flop			
J	K	Q(t + 1)	
0	0	Q(t)	No change
0	1	0	Reset
1	0	1	Set
1	1	Q'(t)	Complement

T flip-flop

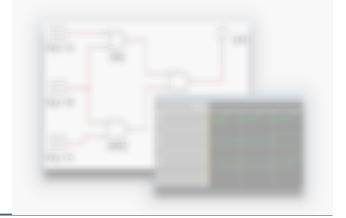

A **T flip-flop** is a flip-flop whose **output toggles between 1 and 0** each applied clock pulse, when an input called T (from toggle) is active.


- The toggle mode of operation of a flip-flop is sometimes useful in synchronous circuits.
- It can be implemented using a DFF.

Χαρακτηριστική εξίσωση


$$Q(t+1) = T \oplus Q = TQ' + T'Q$$

T Flip-Flop


T	Q(t + 1)	
0	Q(t)	No change
1	Q'(t)	Complement

 

(a) From JK flip-flop

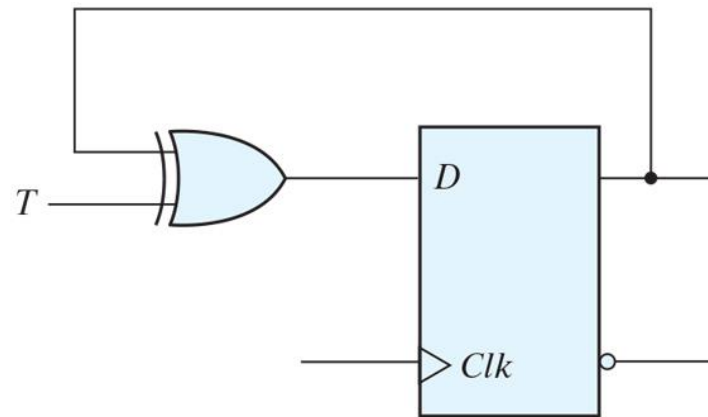


(b) From D flip-flop

 


(c) Graphic symbol

Άμεσες εισοδοι

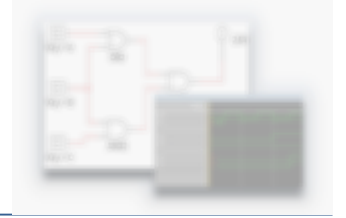

Ορισμένα flip flop διαθέτουν επιπλέον εισόδους, οι οποίες αποκαλούνται **ασύγχρονες εισοδοι**.

 - Η είσοδος που θέτει το flip flop **στο 1** αποκαλείται είσοδος **άμεσης θέσης** (**preset** ή **direct set**)
- Η είσοδος που επαναφέρει το flip flop **στο 0** αποκαλείται είσοδος **άμεσου μηδενισμού** ή **άμεσης επαναφοράς** (**clear** ή **direct reset**).
- Ένα θετικά ακμοπυροδότητο D flip-flop με **ενεργή χαμηλά είσοδο ασύγχρονου μηδενισμού**, παρουσιάζεται παρακάτω.




(b) Graphic symbol


R	Clk	D	Q	Q'
0	X	X	0	1
1	↑	0	0	1
1	↑	1	1	0

(c) Function table

Ευχαριστώ για την προσοχή σας!

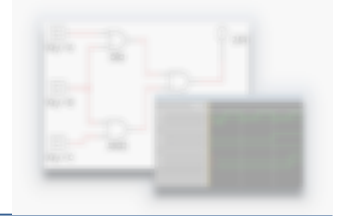

➤ Ερωτήσεις / Απορίες ;

 

Επικοινωνία: ece119.uth@gmail.com